

Register Transfer Language

In this lecture, we will study

- i. Microoperations
- ii. Register Transfer Language and Register Transfer
- iii. Bus and Memory Transfer
- iv. Arithmetic, Logical, and Shift Microoperations
- v. ALU

Chapter Exercises

Microoperations and Register Transfer Language

A Digital System

A digital system is an interconnection of digital hardware modules that accomplish a specific task. These modules are constructed from components like registers, decoders, arithmetic elements, and control logic.

Microoperations

Digital modules are best defined by the **REGISTERS** they contain and the **OPERATIONS** that can be performed on the data stored in these registers.



The operations executed on the data stored in registers are called
MICROOPERATIONS.

Microoperations

So, a microoperation is an elementary operation performed on the information stored in one or more registers.

'Shift', 'load', 'clear', 'count' are all examples of microoperations.

A *bidirectional shift register*, for instance, is capable of performing the 'shift right' and 'shift left' microoperations. Similarly, a *counter with parallel load* is capable of performing 'increment' and 'load' microoperations.

Now that we know what a microoperation is, we can define the internal hardware organization of a digital computer by specifying:

Internal Hardware Organization of a Digital Computer

The set of registers the computer contains

The sequence of microoperations performed on the information stored in the registers

The control that initiates the sequence of microoperations

Register Transfer Language


It is possible to specify the sequence of microoperations by explaining every operation in words, but that would usually involve very lengthy descriptive explanations. It is usually a much better idea to use some sort of symbolic representation to describe the various microoperations.



The symbolic notation used to describe the microoperation transfers among registers is called **REGISTER TRANSFER LANGUAGE**.

Register Transfer Language

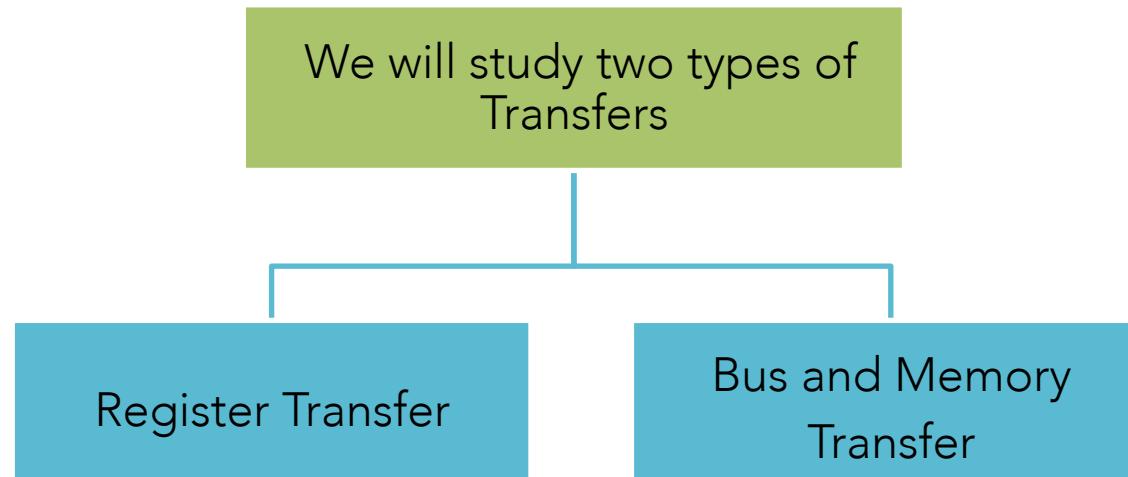The term 'transfer' in Register Transfer Language implies the availability of hardware logic circuits that can perform the stated microoperation and **transfer** the result of the operation to the same or another register.



Registers

Registers: How are they represented?


Computer registers are designated by capital letters (sometimes followed by numerals), which denote the function of the register.

For instance, a register that holds the memory location of data that needs to be accessed is called a *Memory Address Register*, and it is designated as **MAR**.


A *Program Counter* is designated as **PC**

An *Instruction Register* is designated as **IR**, and so forth.


Block Diagram of a Register

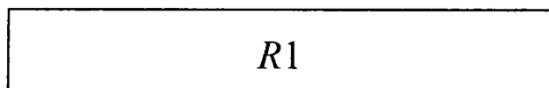


(a) Register R

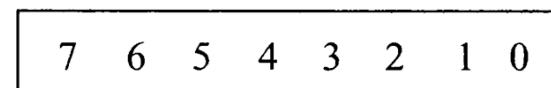

(b) Showing individual bits

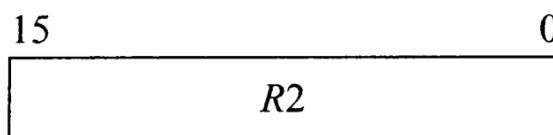

(c) Numbering of bits

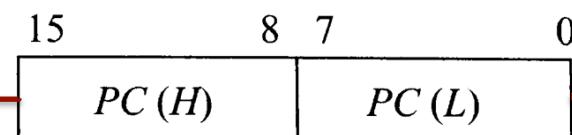

(d) Divided into two parts

'H' implies High-Order Byte
(i.e., bits 8-15)

'L' implies Low-Order Byte
(i.e., bits 0-7)

Register Transfer

Register Transfer

Information transfer from one register to another is designated in symbolic form by means of a replacement operator.

For instance, the statement

$$R2 \leftarrow R1$$

denotes the transfer of the content of register R1 to register R2. In other words, it designates the REPLACEMENT of the content of R2 by the content of R1.

Register Transfer

Normally, we want transfer to occur only under a predetermined control condition. This can be shown by the means of an *if-then* statement.

If (P=1) then (R2 ← R1)

Where P is the control signal generated in the control section.

Control Function


Sometimes, it is convenient to separate the control variables from the register transfer operation by specifying a control function. A control function is a Boolean variable that is equal to 1 or 0.

P: R2 \leftarrow R1

The control condition is terminated with a colon. It symbolizes the requirement that the transfer of the content of R1 into R2 be executed only when P=1.

Block Diagram of a Typical Register Transfer Operation

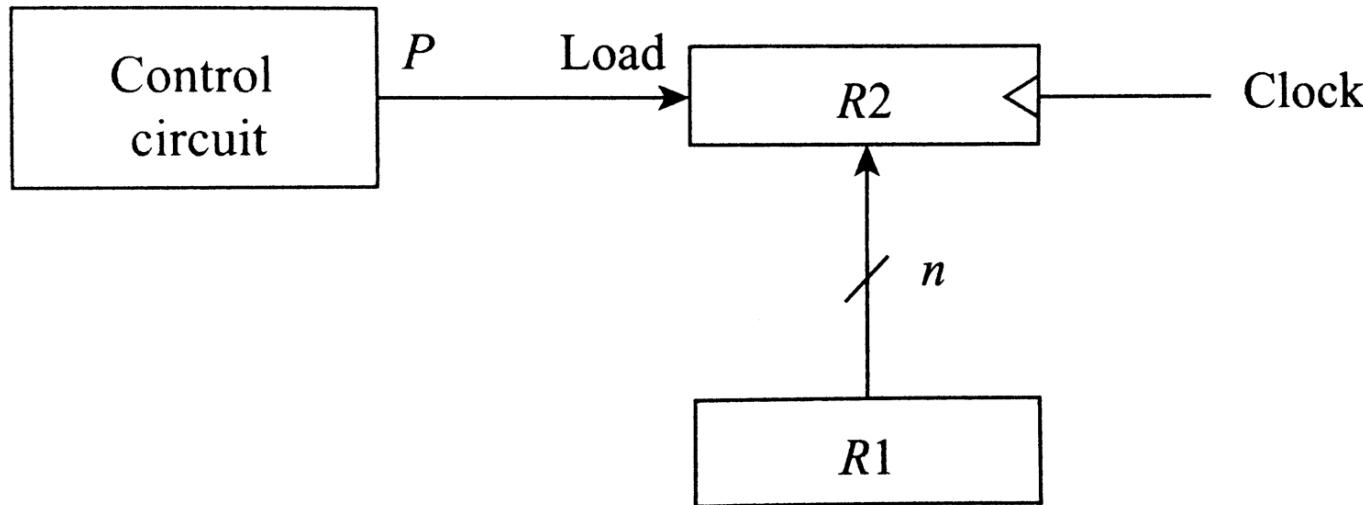When the control variable $P=1$, n bits of data are transferred from $R1$ to $R2$.



Basic Symbols of the Register Transfer Notation

Symbol	Description	Examples
Letters (and numerals)	Denotes a register	$MAR, R2$
Parentheses ()	Denotes a part of a register	$R2(0\text{-}7), R2(L)$
Arrow \leftarrow	Denotes transfer of information	$R2 \leftarrow R1$
Comma ,	Separates two microoperations	$R2 \leftarrow R1, R1 \leftarrow R2$

Exercise

What does the following statement represent?

T: R2 \leftarrow R1, R3 \leftarrow R2

Bus Transfer

Common Bus System

In a typical digital computer with multiple registers, paths must be provided to transfer information from one register to another.



If separate lines of communication are used between each and every register, the number of wires will be excessive.

It is more efficient to use a **COMMON BUS SYSTEM**.


Common Bus

A bus consists of a set of common lines – one for each bit of a register
– through which binary information is transferred one at a time.




A control signal determines which register is selected by the bus
during a particular register transfer.

Bus System for Four Registers

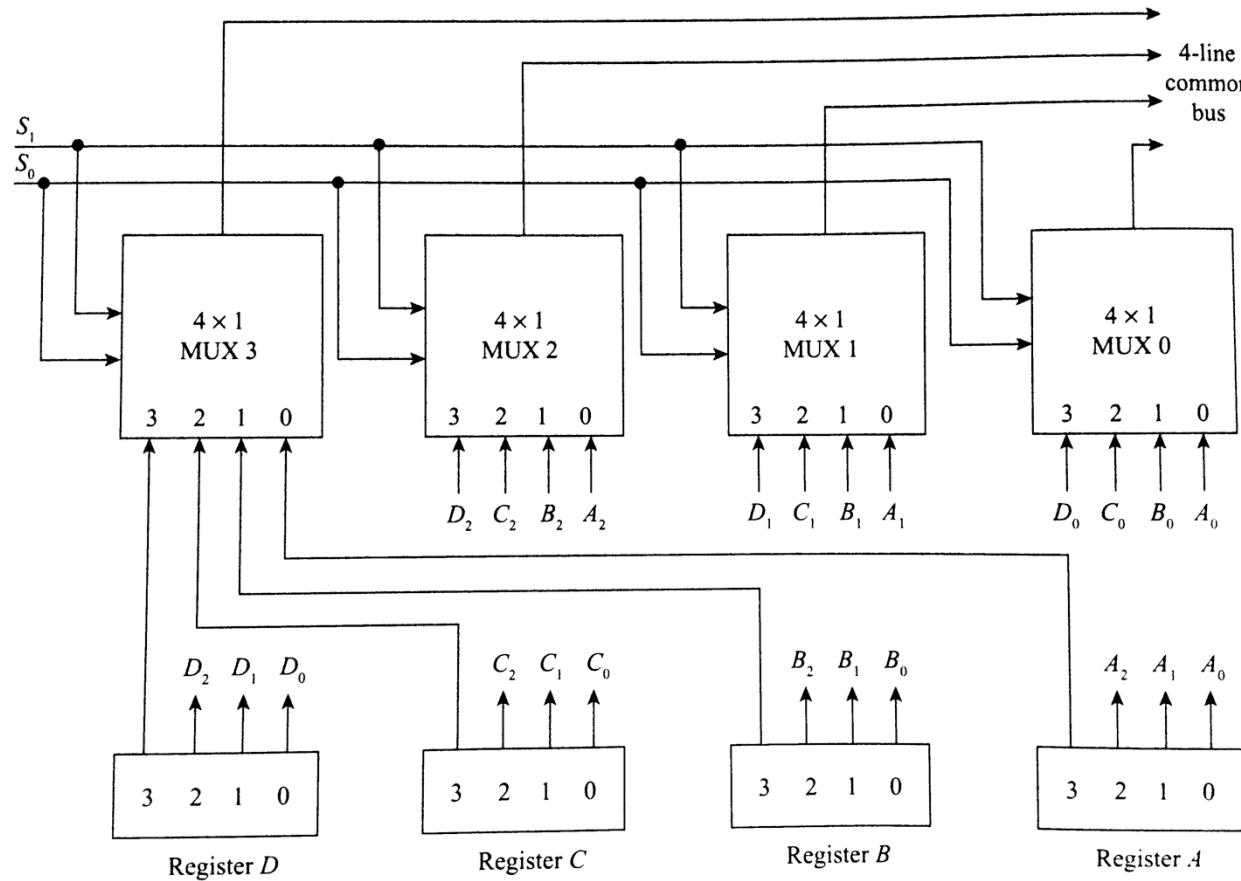

Bus System for Four Registers

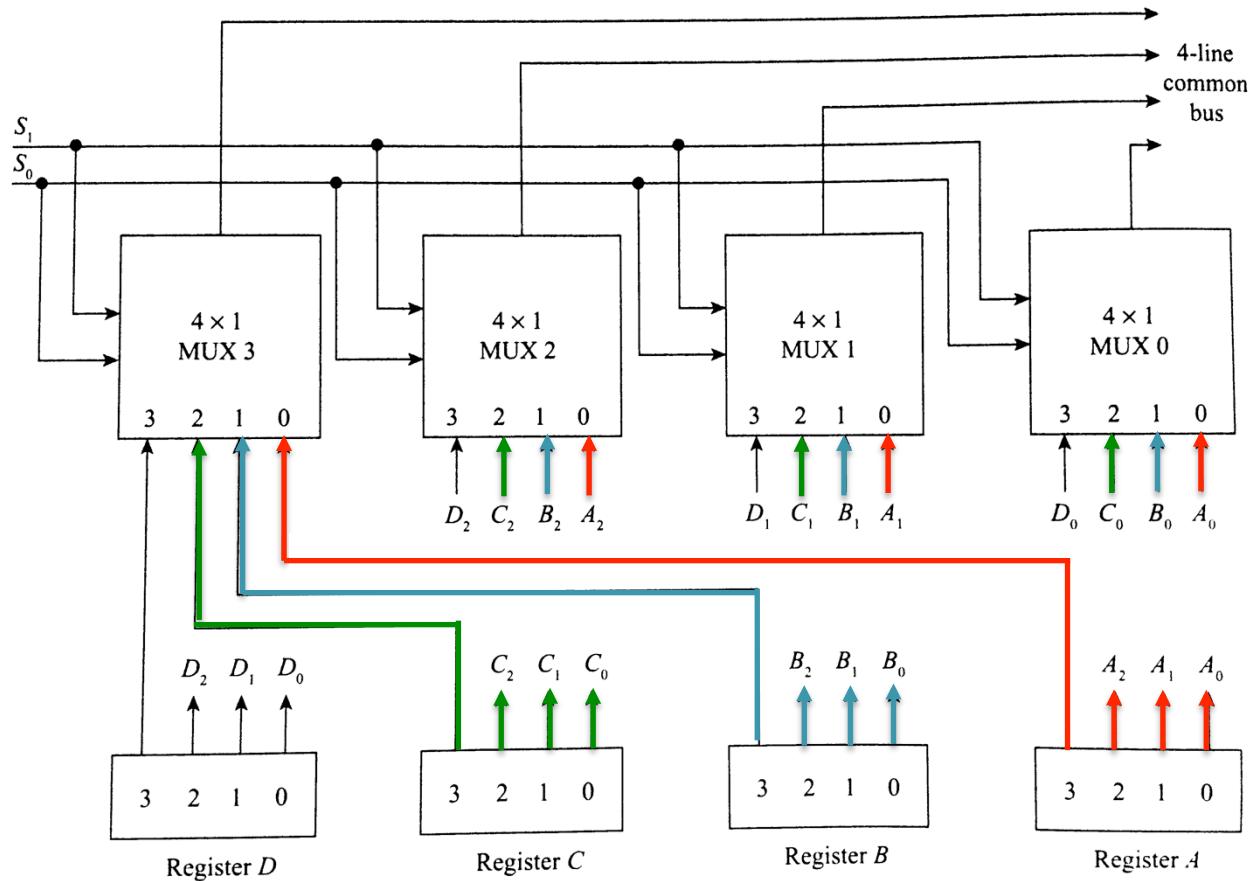

S0	S1	Register Selected
0	0	A
0	1	B
1	0	C
1	1	D

Function Table

Bus-Based Register Transfer

When the bus is included, register transfer is symbolized as follows:

T: BUS \leftarrow C, R1 \leftarrow BUS


This statement implies that the contents of register C are placed on the bus and the contents of the bus are then loaded into register R1 by activating the load control input T.

If the bus is known to exists in the system,
the previous statement can be simply written as:


R1 \leftarrow C

Three-State Bus Buffers

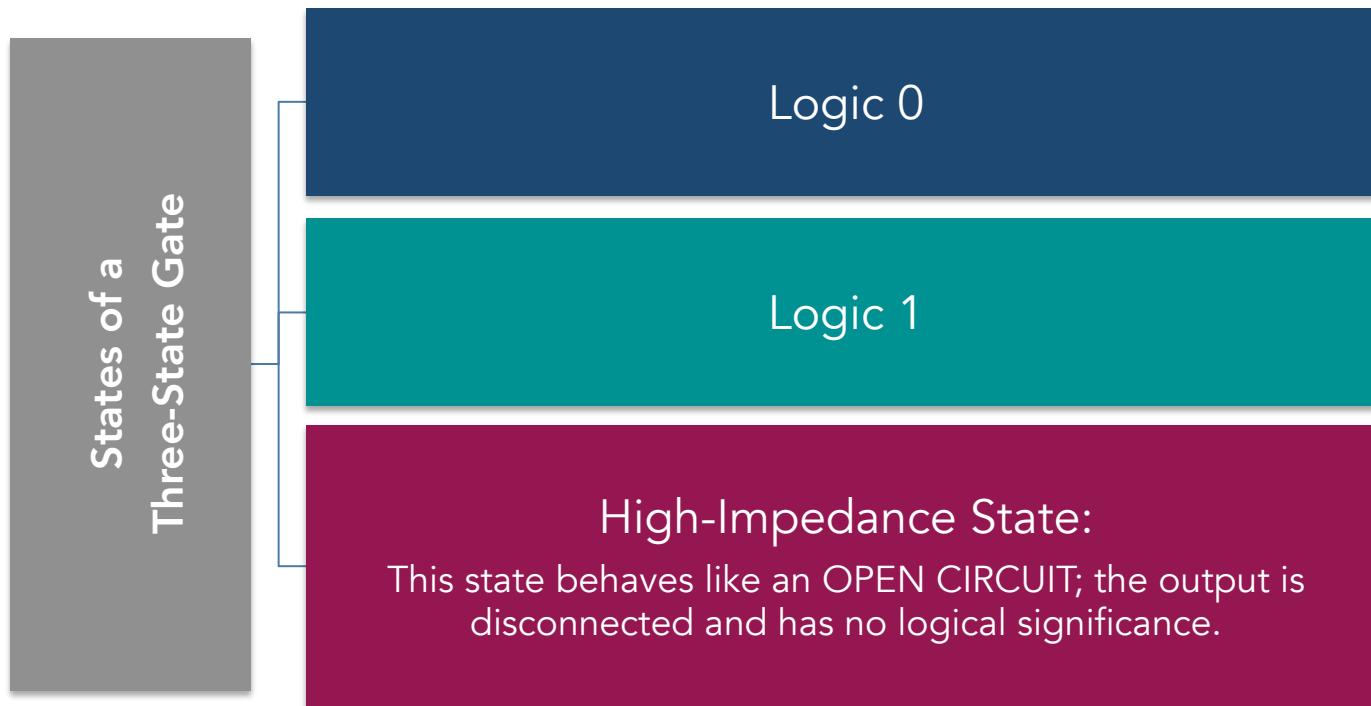A bus system can be constructed with three-state gates instead of multiplexers.




Graphical Symbol of a Three-State Buffer

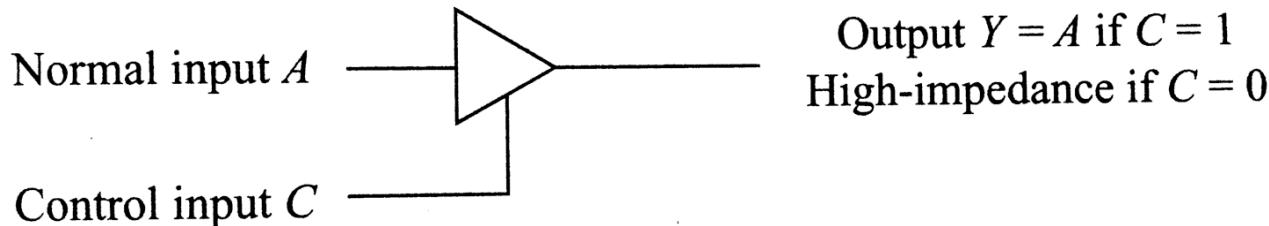

Unlike regular buffer gates, a three-state buffer has an additional control input C ;
 C determines the output state of the buffer.

When $C=1$, the output is enabled and the gate behaves like a conventional buffer.
When $C=0$, the output is disabled and the gate goes into a high-impedance state.

Bus Line With Three-State Buffers

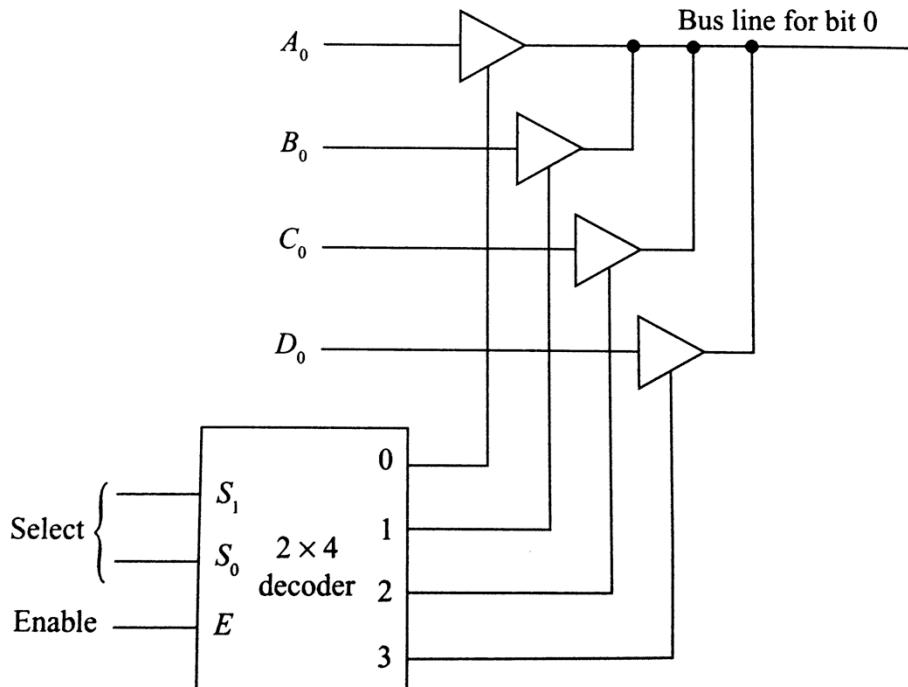

Only one of the four three-state buffers should be active at any given time. One way to achieve that is to use a decoder.

When Enable input of the decoder is 0, all of its outputs will be 0, i.e., all the three-state buffers will be inactive.

When $E=1$, any one of the three-state buffers will become active, depending on the values of the Select inputs.

Exercise

Can we build a bus system using a gate other than the buffer?

If yes, how? If not, why?

Memory Transfer

Memory Transfer Operations

READ OPERATION

Transfer of information from a memory word to the outside environment

WRITE OPERATION

Transfer of new information to be stored into the memory

Symbolic Representation of a READ Operation

Consider a memory unit that receives the address from a register, called the address register (AR), and the data is to be transferred into another register called the data register (DR).

The READ operation can be stated as follows:

Read: DR \leftarrow M[AR]

This causes a transfer of information from the memory word M selected by the address in AR into DR.

Symbolic Representation of a WRITE Operation

A write operation transfers the contents of a register (say R1) to a memory word M selected by the address present in the address register (say AR).

The WRITE operation can be stated symbolically as :

Write: $M[AR] \leftarrow R1$

This causes a transfer of information from R1 into the memory word M selected by the address in AR.

Microoperations

Types of Microoperations

Register Transfer Microoperations

Arithmetic Microoperations

Logic Microoperations


Shift Microoperations

Arithmetic Microoperations

Symbolic designation	Description
$R3 \leftarrow R1 + R2$	Contents of $R1$ plus $R2$ transferred to $R3$
$R3 \leftarrow R1 - R2$	Contents of $R1$ minus $R2$ transferred to $R3$
$R2 \leftarrow \overline{R2}$	Complement the contents of $R2$ (1's complement)
$R2 \leftarrow \overline{R2} + 1$	2's complement the contents of $R2$ (negate)
$R3 \leftarrow R1 + \overline{R2} + 1$	$R1$ plus the 2's complement of $R2$ (subtraction)
$R1 \leftarrow R1 + 1$	Increment the contents of $R1$ by one
$R1 \leftarrow R1 - 1$	Decrement the contents of $R1$ by one


4-Bit Binary Adder

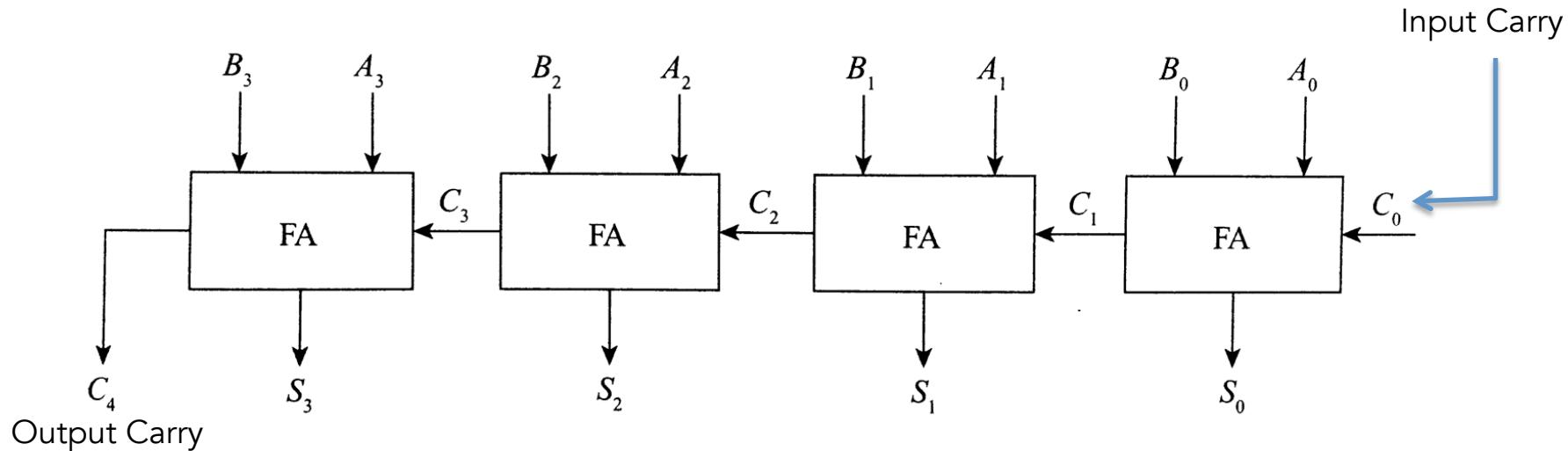Bits A_0, A_1, A_2 , and A_3 come from one register (such as R1) and Bits B_0, B_1, B_2 , and B_3 come from another register (such as R2).



Bits S_0, S_1, S_2 , and S_3 together form the required sum.

Binary Adder–Subtractor

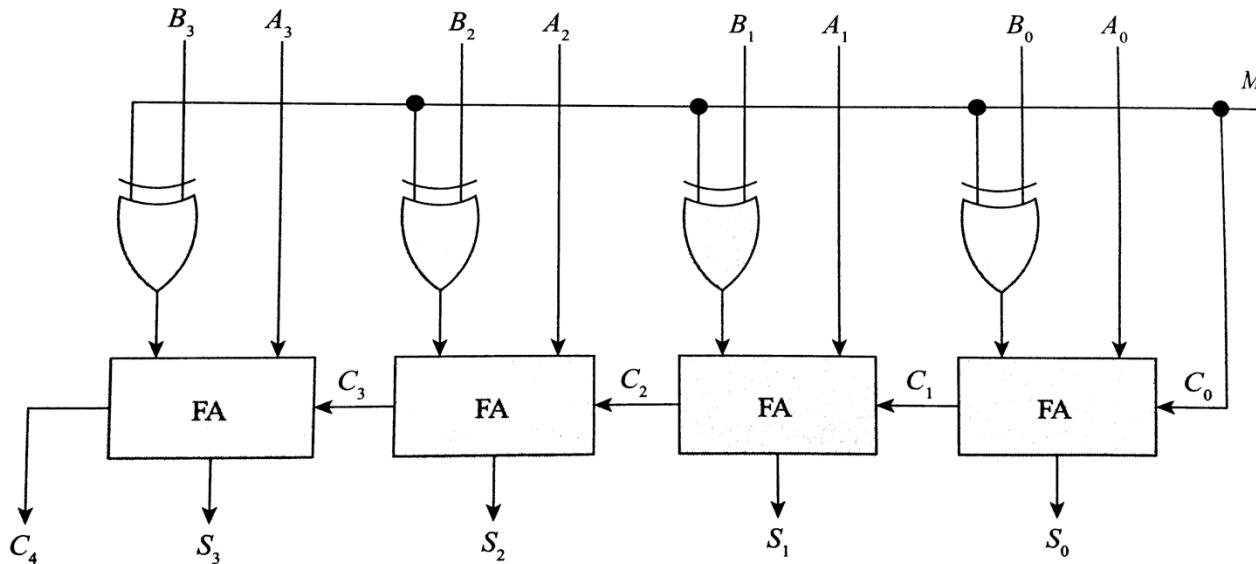


M is the mode of the circuit

When $M=0$, the circuit becomes an adder

When $M=1$, the circuit becomes a subtractor


4-Bit Binary Incrementer

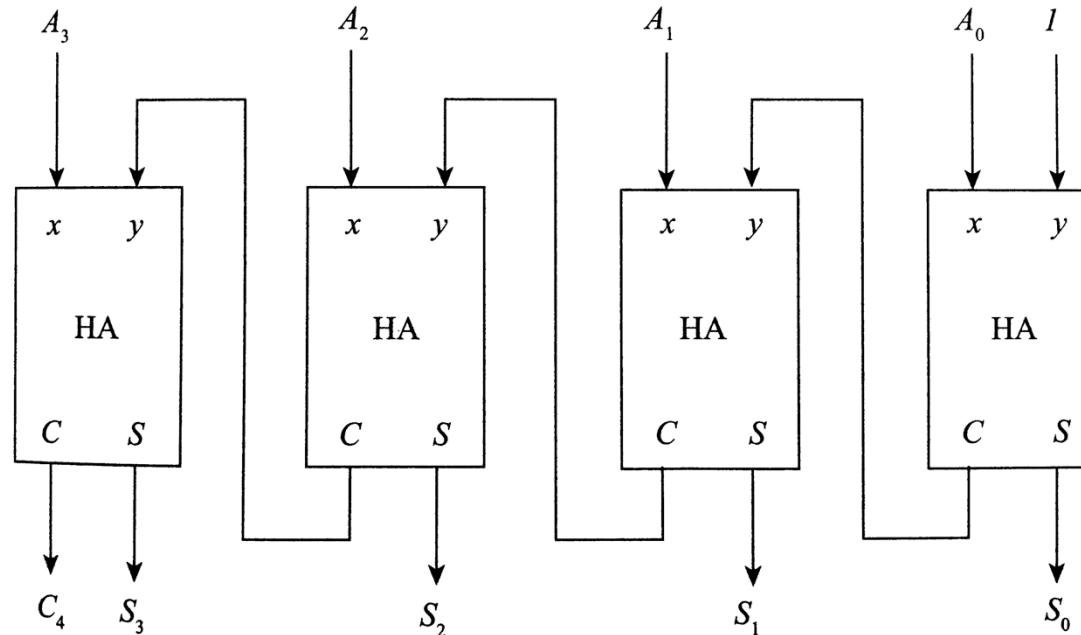

The increment microoperation adds 1 to a number in a register.

Arithmetic Circuit

Select			Input	Output	
S_1	S_0	C_{in}	Y	$D = A + Y + C_{in}$	Microoperation
0	0	0	B	$D = A + B$	Add
0	0	1	B	$D = A + B + 1$	Add with carry
0	1	0	\bar{B}	$D = A + \bar{B}$	Subtract with borrow
0	1	1	\bar{B}	$D = A + \bar{B} + 1$	Subtract
1	0	0	0	$D = A$	Transfer A
1	0	1	0	$D = A + 1$	Increment A
1	1	0	1	$D = A - 1$	Decrement A
1	1	1	1	$D = A$	Transfer A

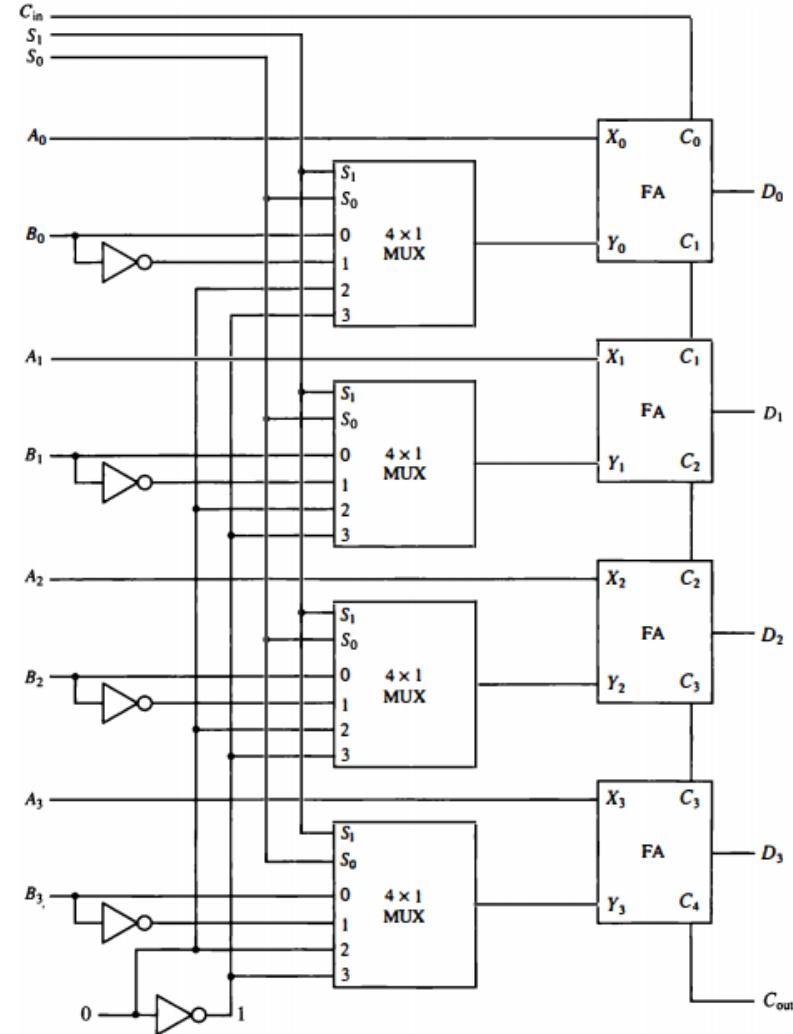

Logic Microoperations

Logic microoperations specify binary operations that can be performed on strings of bits stored in registers.

These operations consider each bit of the register separately and treat them as binary variables, which is why, they are considered to be bit-wise operations.

Logic Microoperations

For instance, the XOR microoperation with the contents of two registers R1 and R2 is symbolized by the statement

$$P: R1 \leftarrow R1 \oplus R2$$

The XOR microoperation is performed on the individual bits of the registers, provided that the control variable $P = 1$.

Logic Microoperations: Example

Let the contents of R1 be 1010 and the contents of R2 be 1100.

The XOR microoperation **P: R1 $\leftarrow R1 \oplus R2$**

symbolizes the following operation:

1010 Contents of R1

1100 Contents of R2

0110 Contents of R1 after P=1

List of Logic Microoperations

Boolean function	Microoperation	Name	Boolean function	Microoperation	Name
$F_0 = 0$	$F \leftarrow 0$	Clear	$F_8 = (x + y)'$	$F \leftarrow \overline{A \vee B}$	NOR
$F_1 = xy$	$F \leftarrow A \wedge B$	AND	$F_9 = (x \oplus y)'$	$F \leftarrow \overline{A \oplus B}$	Exclusive-NOR
$F_2 = xy'$	$F \leftarrow A \wedge \overline{B}$		$F_{10} = y'$	$F \leftarrow \overline{B}$	Complement B
$F_3 = x$	$F \leftarrow A$	Transfer A	$F_{11} = x + y'$	$F \leftarrow A \vee \overline{B}$	
$F_4 = x'y$	$F \leftarrow \overline{A} \wedge B$		$F_{12} = x'$	$F \leftarrow \overline{A}$	Complement A
$F_5 = y$	$F \leftarrow B$	Transfer B	$F_{13} = x' + y$	$F \leftarrow \overline{A} \vee B$	
$F_6 = x \oplus y$	$F \leftarrow A \oplus B$	Exclusive-OR	$F_{14} = (xy)'$	$F \leftarrow \overline{A \wedge B}$	NAND
$F_7 = x + y$	$F \leftarrow A \vee B$	OR	$F_{15} = 1$	$F \leftarrow \text{all } 1\text{'s}$	Set to all 1's

Important Note

When the symbol + occurs in a microoperation, it will denote an arithmetic plus. But when it occurs in a control (or Boolean) function, it will denote an OR operation.


For instance, in the following statement:

$$P + Q: R1 \leftarrow R2 + R3, R4 \leftarrow R5 \vee R6$$

OR operation between two binary variables of a control function ADD microoperation OR microoperation

Hardware Implementation of Logic Microoperations

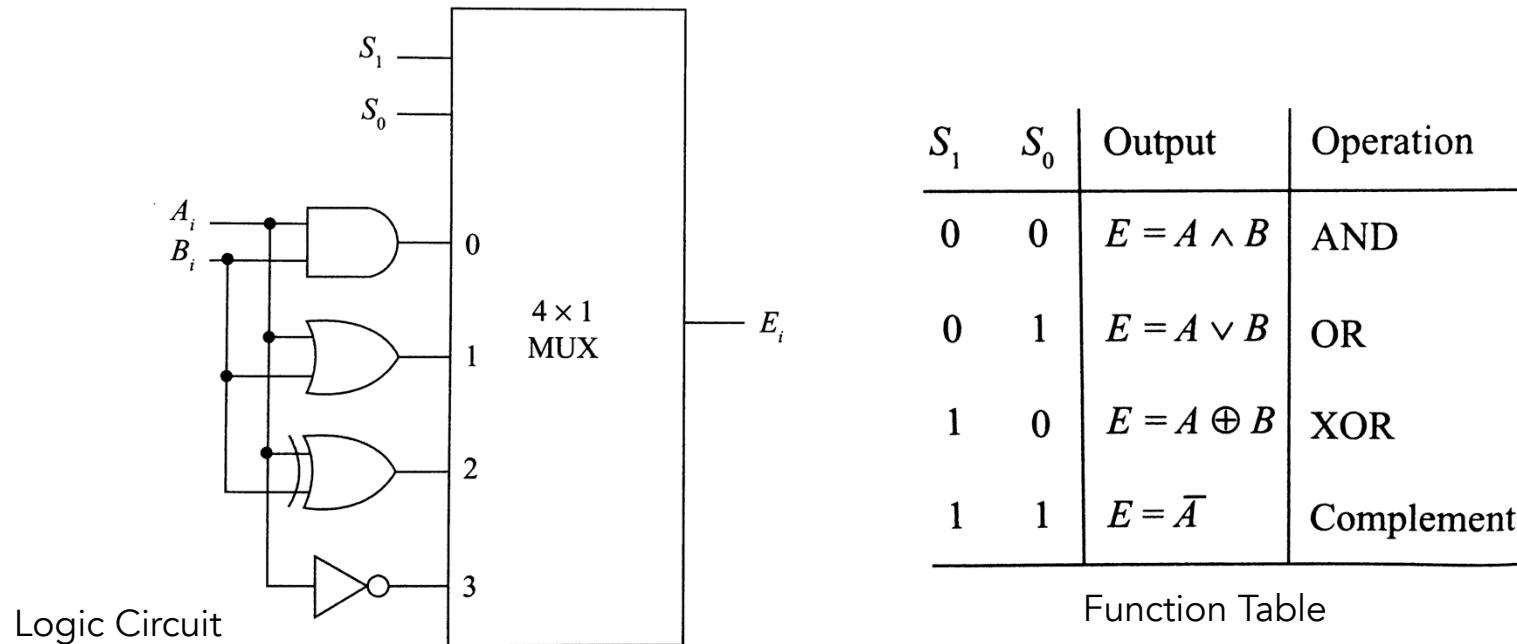Although there are 16 logic microoperations, most computers use only 4 – AND, OR, XOR, and COMPLEMENT – from which, all others can be derived.



Some Applications of Logic Microoperations

Logic microoperations are very useful for manipulating individual bits or portions of a word stored in a register.

Selective-Set Operation: This operation sets to 1 the bits in register A where there are corresponding 1s in register B. For instance,

$$\begin{array}{r} 1010 \quad \text{A (before)} \\ 1100 \quad \text{B (logical operand)} \\ \hline 1110 \quad \text{A (after selective-set)} \end{array}$$

Some Applications of Logic Microoperations

Selective-Complement Operation: This operation complements the bits in register A where there are corresponding 1s in register B. It does not affect bit positions that have 0s in B. For instance,

$$\begin{array}{rcl} 1 & 0 & 1 & 0 & \text{A (before)} \\ 1 & 1 & 0 & 0 & \text{B (logical operand)} \\ \hline 0 & 1 & 1 & 0 & \text{A (after selective-complement)} \end{array}$$

Some Applications of Logic Microoperations

Selective-Clear Operation: This operation clears to 0 the bits in A only when there are corresponding 1s in B. For instance,

$$\begin{array}{r} 1010 \quad A \text{ (before)} \\ 1100 \quad B \text{ (logical operand)} \\ \hline 0010 \quad A \text{ (after selective-clear)} \end{array}$$

The corresponding microoperation is $A \leftarrow A \wedge \overline{B}$

Some Applications of Logic Microoperations

Mask Operation: This operation is similar to the selective-clear operation, except that the bits of A are cleared to 0 only when there are corresponding 0s in B. For instance,

$$\begin{array}{r} 1010 \quad \text{A (before)} \\ 1100 \quad \text{B (logical operand)} \\ \hline 1000 \quad \text{A (after masking)} \end{array}$$

Some Applications of Logic Microoperations

Insert Operation: This operation inserts a new value into a group of bits. This is done by first masking the bits and then ORing them with the required value. For instance, suppose A contains 8 bits: 0110 1010. To replace the four leftmost bits by 1001, we first mask the four unwanted bits:

0 1 1 0 1 0 1 0	A (before)
0 0 0 0 1 1 1 1	B (mask)
0 0 0 0 1 0 1 0	A (after masking)

And then inserting the new value:

0 0 0 0 1 0 1 0	A (before)
1 0 0 1 0 0 0 0	B (insert)
1 0 0 1 1 0 1 0	A (after insertion)

Some Applications of Logic Microoperations

Clear Operation: This operation compares the words in A and B and produces an all 0 result if the two numbers are equal.
(This is done using the XOR microoperation.)

$$\begin{array}{r} 1010 \quad A \\ 1010 \quad B \\ \hline 0000 \quad A \leftarrow A \oplus B \end{array}$$

Shift Microoperations

Shift microoperations are used for serial transfer of data.

The contents of a register can be shifted either to the left or to the right.

There are three types of shifts:

- > Logical
- > Circular
- > Arithmetic

Logical Shift

Logical shift transfers 0 through the serial input.

For instance, the microoperation

R1 \leftarrow shl R1

indicates a 1-bit shift to the left of the contents of register R1

and

R2 \leftarrow shr R2

indicates a 1-bit shift to the right of the contents of register R2.

Example of Logical Shift-Left

The leftmost bit
is discarded



1 0 0 1 1 0 0 1

R1 (before)

/ / / / / / /
0 0 1 1 0 0 1 0

R1 (after logical shift-left)



An extra 0 is added
to the right

Example of Logical Shift-Right

The rightmost bit
is discarded



1 0 0 1 1 0 0 1

R1 (before)

0 1 0 0 1 1 0 0

R1 (after logical shift-right)



An extra 0 is added
to the left

Circular Shift aka Rotation Operation

Circular shift circulates the bits of the register around the two ends without loss of information.

The microoperation

$$R1 \leftarrow cil R1$$


indicates a 1-bit circular shift to the left of the contents of R1
and

$$R2 \leftarrow cir R2$$

indicates a 1-bit circular shift to the right of contents of R2.

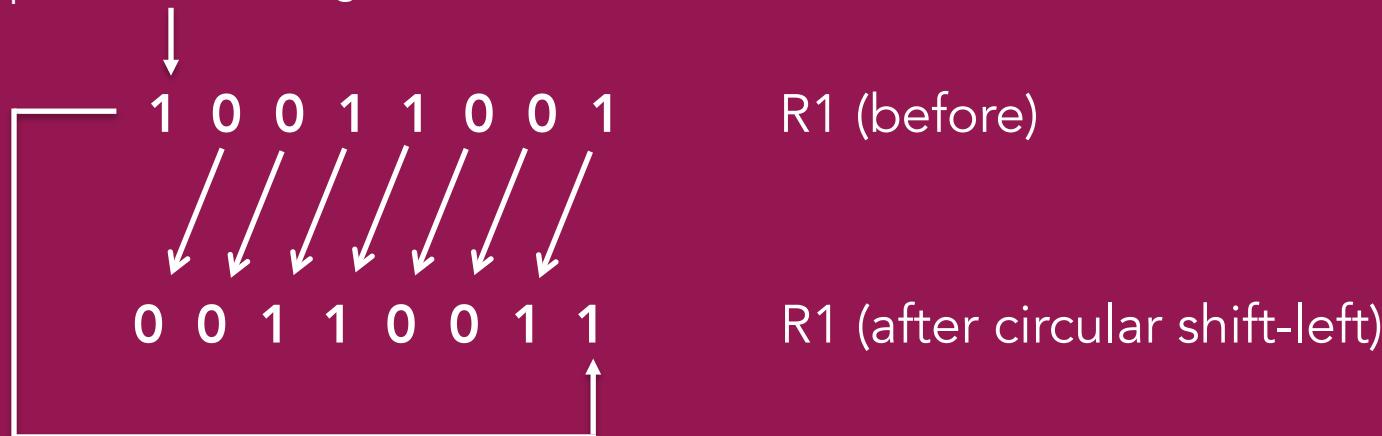
Example of Circular Shift-Left

The leftmost bit
is moved to the empty
position on the right



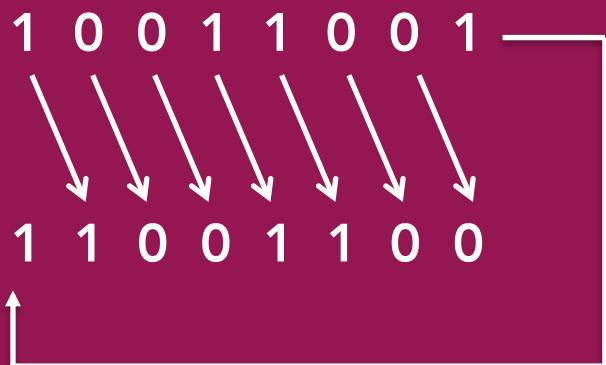Example of Circular Shift-Right

The rightmost bit
is moved to the empty
position on the left



R1 (before)

R1 (after circular shift-right)

Arithmetic Shift

This shifts a **signed binary number** to the left or right.

The microoperation

$$R1 \leftarrow \text{ashl } R1$$

multiples a signed binary number by 2

and

$$R2 \leftarrow \text{ashr } R2$$


divides a signed binary number by 2.

The sign bit (i.e., the leftmost bit) must remain unchanged.

Example of Arithmetic Shift-Right

The leftmost bit is the sign bit, and it must remain unchanged.

The rightmost bit is discarded

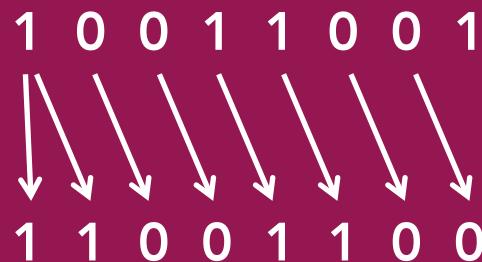

R1 (before)

R1 (after arithmetic shift-right)

Example of Arithmetic Shift-Left

The leftmost bit
discarded.



Caveats of Arithmetic Shift-Left


Arithmetic shift-left can cause the sign bit to be lost, which means that a number, which was originally negative, could become positive after the shift, and vice versa. This may result in the generation of erroneous results.

The lost sign bit is generally treated as “overflow”. In other words, if an arithmetic shift-left operation causes the sign of the given number to change, overflow occurs.

1 0 0 1 1 0 0 1 R1 (negative number)

0 0 1 1 0 0 1 0 R1 (becomes positive after the shift)

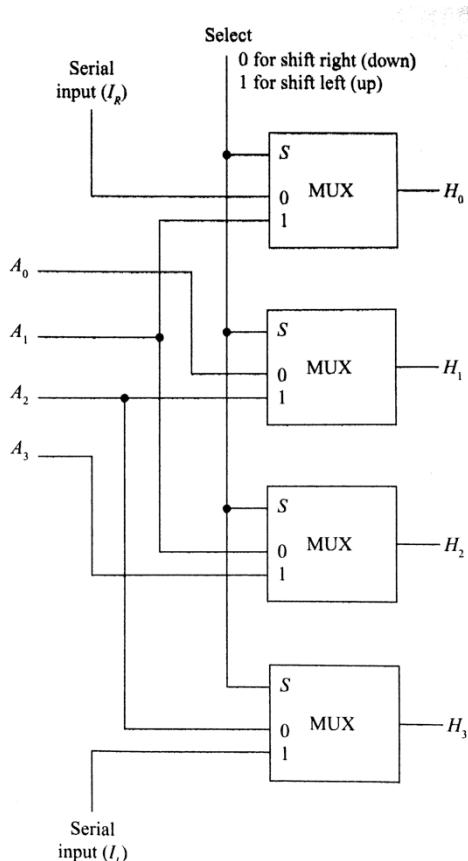Hardware Implementation of a Circuit Shifter



4-bit Combinational Circuit Shifter

Select	Output			
	H_0	H_1	H_2	H_3
0	I_R	A_0	A_1	A_2
1	A_1	A_2	A_3	I_L

Function Table

Exercise

Which category of microoperations does not manipulate the actual information content of a register?


Arithmetic Logic Shift Unit

Arithmetic Logic Shift Unit

The arithmetic, logic, and shift circuits that we examined previously can all be combined into one single Arithmetic Logic Shift Unit with common selection variables.

That way, a single circuit can perform all these operations.

Arithmetic Logic Shift Unit

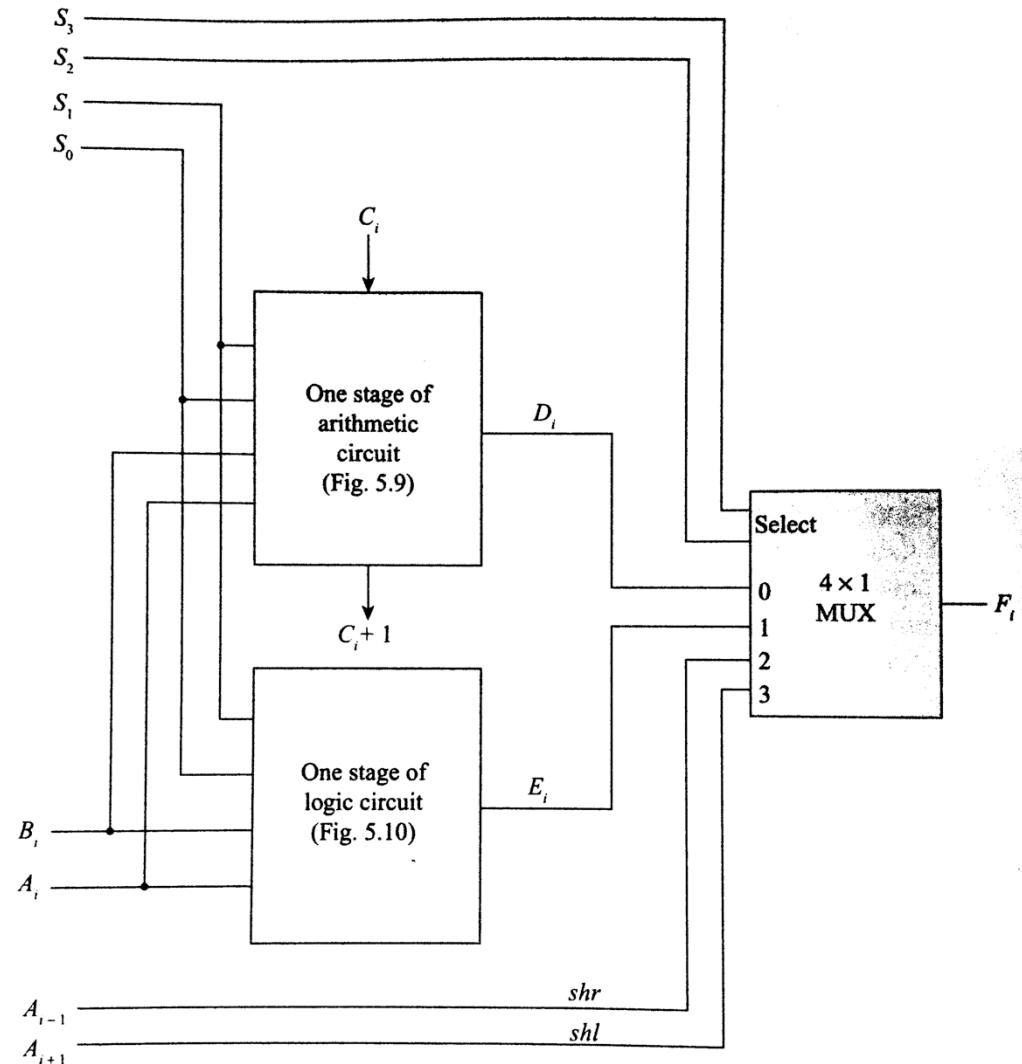

Function Table for
Arithmetic Logic Shift Unit

Operation select							
S_3	S_2	S_1	S_0	C_{in}	Operation	Function	
0	0	0	0	0	$F = A$	Transfer A	
0	0	0	0	1	$F = A + 1$	Increment A	
0	0	0	1	0	$F = A + B$	Addition	
0	0	0	1	1	$F = A + B + 1$	Add with carry	
0	0	1	0	0	$F = A + \bar{B}$	Subtract with borrow	
0	0	1	0	1	$F = A + \bar{B} + 1$	Subtraction	
0	0	1	1	0	$F = A - 1$	Decrement A	
0	0	1	1	1	$F = A$	Transfer A	
0	1	0	0	X	$F = A \wedge B$	AND	
0	1	0	1	X	$F = A \vee B$	OR	
0	1	1	0	X	$F = A \oplus B$	XOR	
0	1	1	1	X	$F = \bar{A}$	Complement A	
1	0	X	X	X	$F = \text{shr } A$	Shift right A into F	
1	1	X	X	X	$F = \text{shl } A$	Shift left A into F	




Exercises

1. Show the block diagram of the hardware that implements the following register transfer statement:

$$yT2: R2 \leftarrow R1, R1 \leftarrow R2$$

Solution:

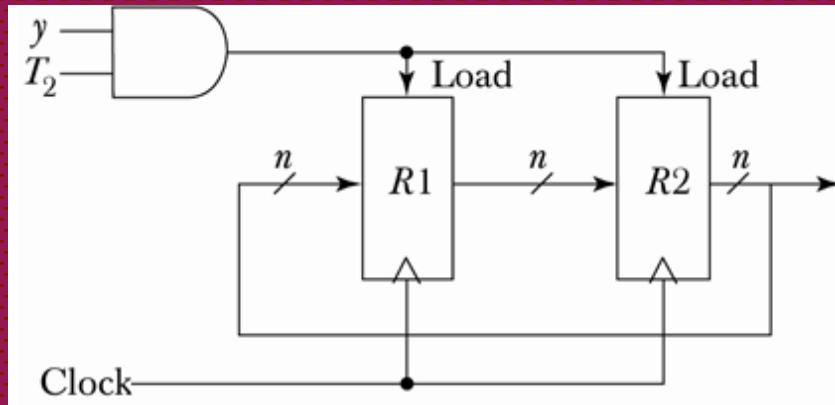

2. The outputs of four registers R_0 , R_1 , R_2 , and R_3 are connected through 4-to-1 line multiplexer to the inputs of the fifth register, R_5 . Each register is 8 bits long. The required transfers are dictated by four timing variables T_0 to T_3 as follows:

$$T_0: R_5 \leftarrow R_0$$

$$T_1: R_5 \leftarrow R_1$$

$$T_2: R_5 \leftarrow R_2$$

$$T_3: R_5 \leftarrow R_3$$

The timing variables are mutually exclusive. Draw a block diagram showing the hardware implementation of the register transfers.

Include the necessary connections from the four timing variables to the selection inputs of the mux and to the load input of register R_5 .

Solution: Step 1


$R0$

$R1$


$R2$

$R3$

Solution: Step 2

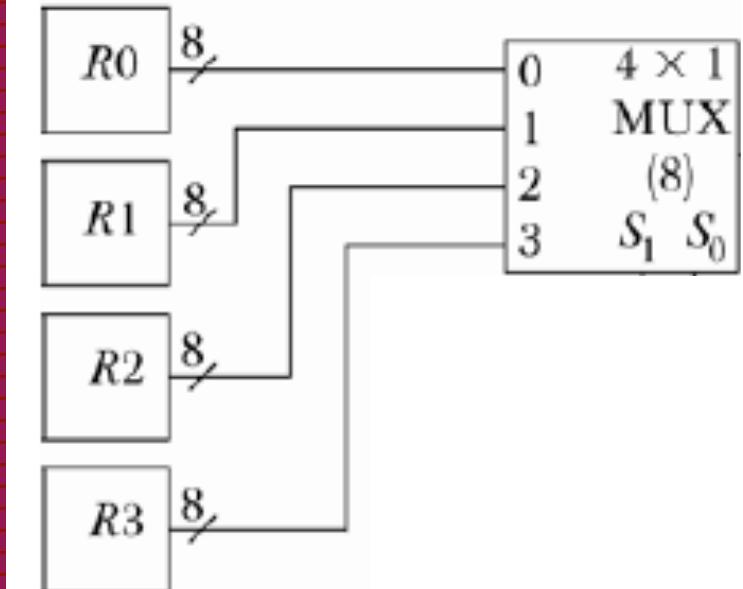

Solution: Step 3

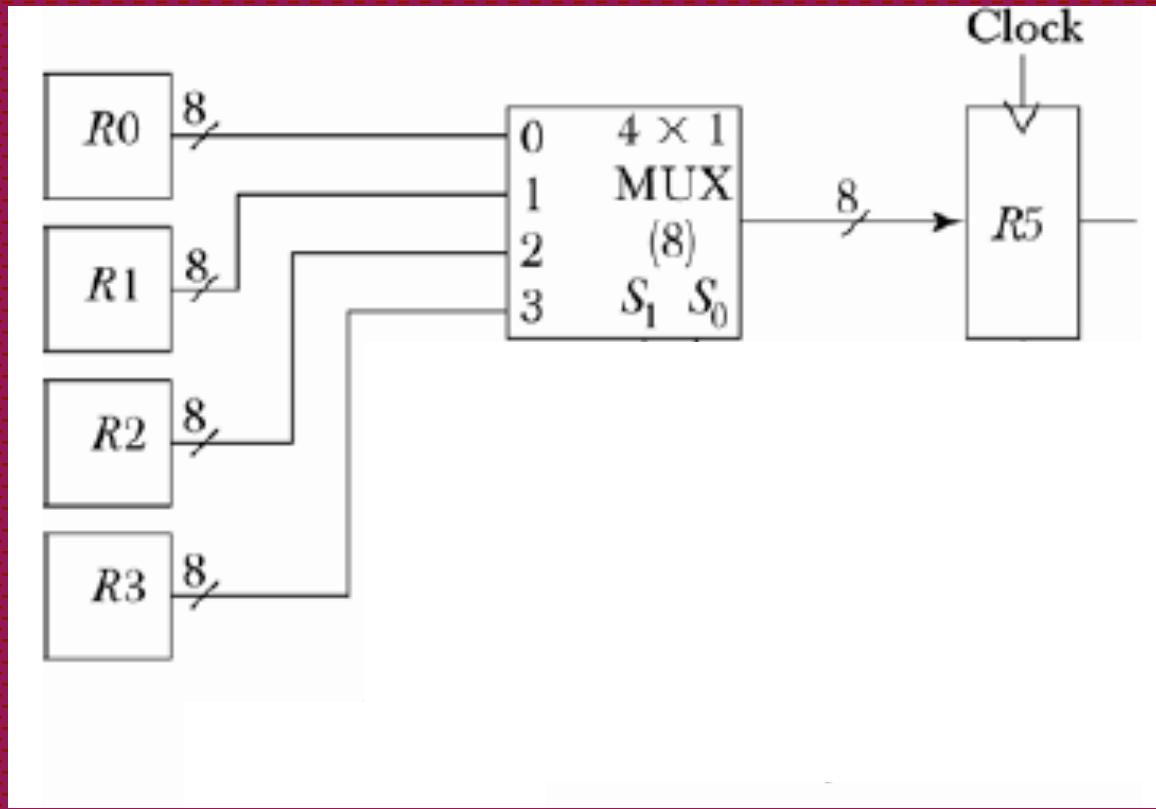


Solution: Step 4

The two selection inputs of the mux (i.e., S_1 and S_0), will help determine which of the four registers will be able to load their contents into R5.

Each register transfer is further controlled by a timing signal (at T_0 , R0 will transfer its contents to R5. At T_1 , R1 will transfer its contents to R5. And so on).

So now, we need to find a way to convert the four timing signals (T_0 , T_1 , T_2 , and T_3) into the mux's selection inputs S_1 and S_0 .

Solution: Step 4

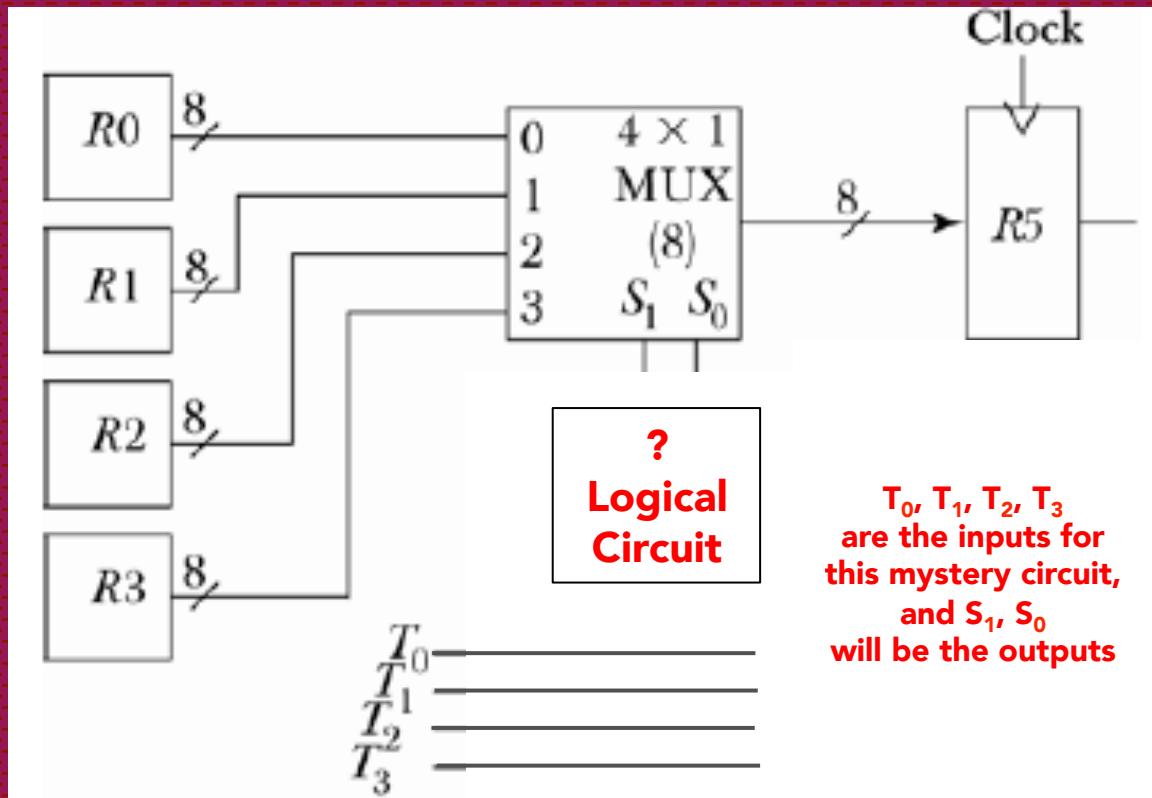

Solution: Step 4

Our mux has four inputs (one from each of the four registers). One of these inputs will become the output, depending on the combination of S_1 and S_0 .

S_1	S_0	The input from which register will become the output	Which timing signal which allow this register to transfer data
0	0	R0	T_0
0	1	R1	T_1
1	0	R2	T_2
1	1	R3	T_3

Solution: Step 4

Inputs to the mystery circuit

Outputs of the mystery circuit

The previous truth table can be written as:

Timing Signals	S_1	S_0	Output of the mux
$T_0 \ T_1 \ T_2 \ T_3$			
0 0 0 0	X	X	-
1 0 0 0	0	0	R0
0 1 0 0	0	1	R1
0 0 1 0	1	0	R2
0 0 0 1	1	1	R3

Solution: Step 4

We have a truth table that provides the values of S_1 and S_0 corresponding to the values of T_0 , T_1 , T_2 , and T_3 .

Now we need to find simplified expressions that represent these relationships.

We'll use K-maps.

Solution: Step 5

K-Map for S_1

		T_2, T_3	00	01	11	10
		00	x	1		1
		01	0			
		11				
		10	0			


Solution: Step 5

		00	01	11	10
		T ₀ , T ₂	T ₁ , T ₃		
00	01	x	1	x	1
		0			
11					
10		0			


$$S_0 = T_0' T_2'$$

Solution: Step 5

Simplified K-Maps for S_1

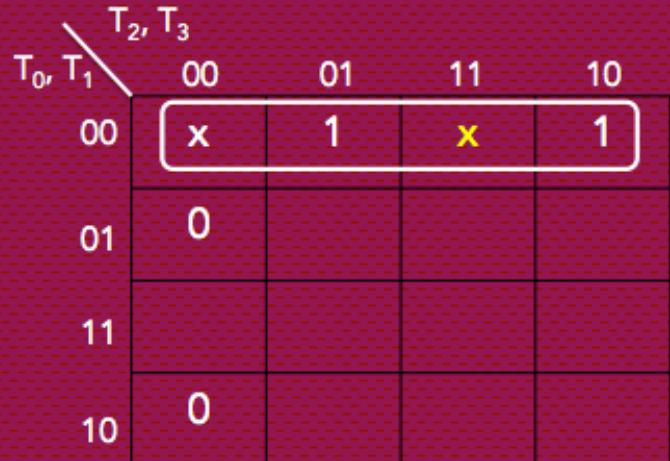

OR

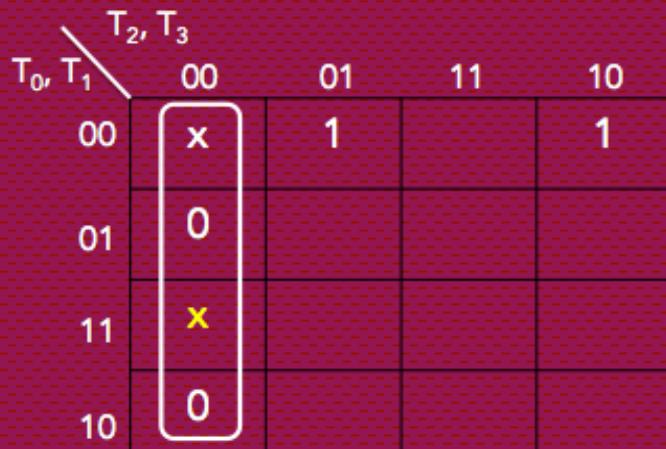

$$S_1 = T_0'T_1'$$

$$S_1 = T_2 + T_3 \text{ (POS)}$$

Solution: Step 6

K-Map for S_0

		T_2, T_3	00	01	11	10
		00	x	1		0
		01	1			
		11				
		10	0			

Solution: Step 6

Alternative K-Map for S_0


		00	01	11	10
		00	x	1	1
		01	0		
		11			
		10	0		

T_1, T_3


T_0, T_2

Solution: Step 5

Simplified Alternative K-Maps for S_0

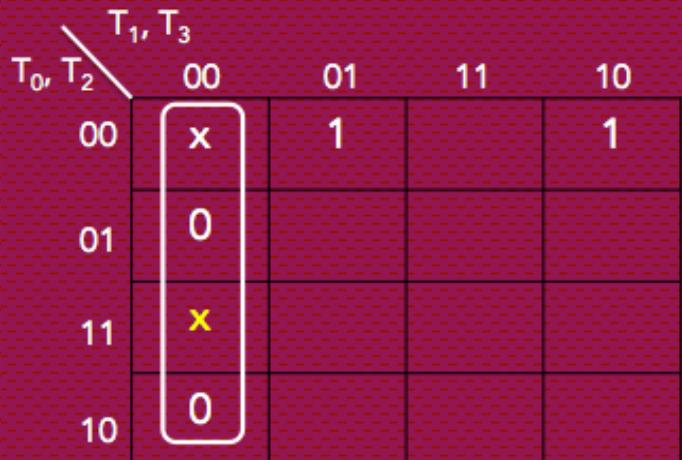

OR

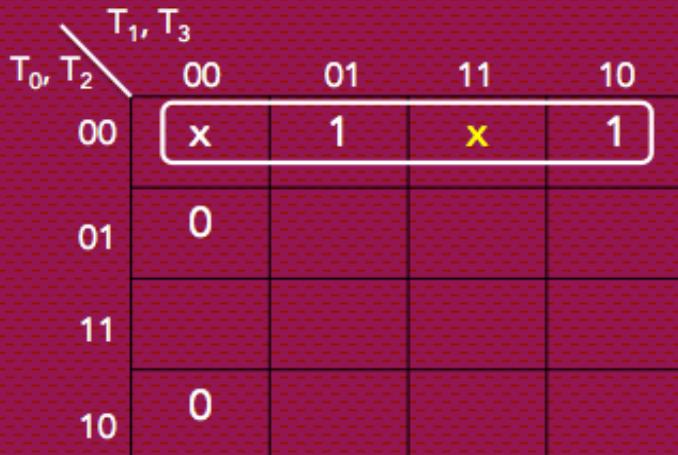

$$S_0 = T_1 + T_3 \text{ (POS)}$$


$$S_0 = T_0'T_2'$$

Solution: Step 5


Crosscheck your answer

Timing Signals				S_1	S_0	$S_1 = T_2 + T_3$	$S_0 = T_1 + T_3$
T_0	T_1	T_2	T_3				
1	0	0	0	0	0	$0 + 0 = 0$	$0 + 0 = 0$
0	1	0	0	0	1	$0 + 0 = 0$	$1 + 0 = 1$
0	0	1	0	1	0	$1 + 0 = 1$	$0 + 0 = 0$
0	0	0	1	1	1	$0 + 1 = 1$	$0 + 1 = 1$


Solution: Step 6

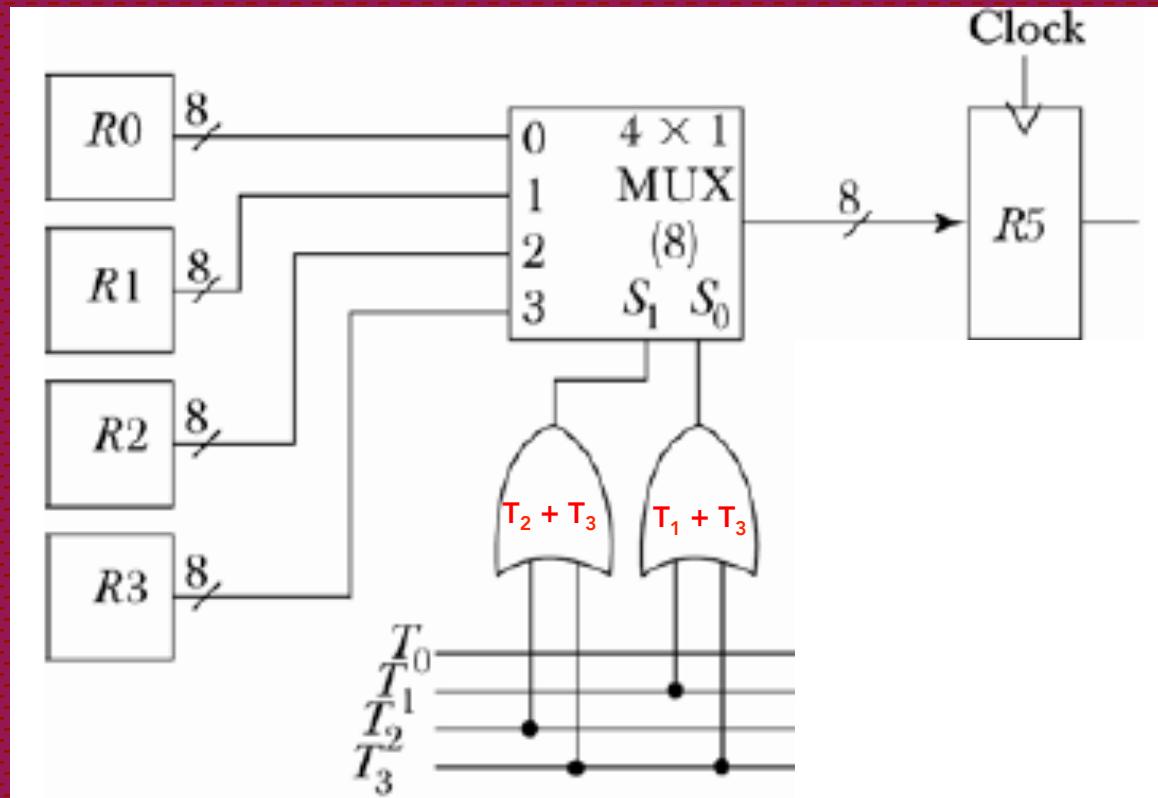

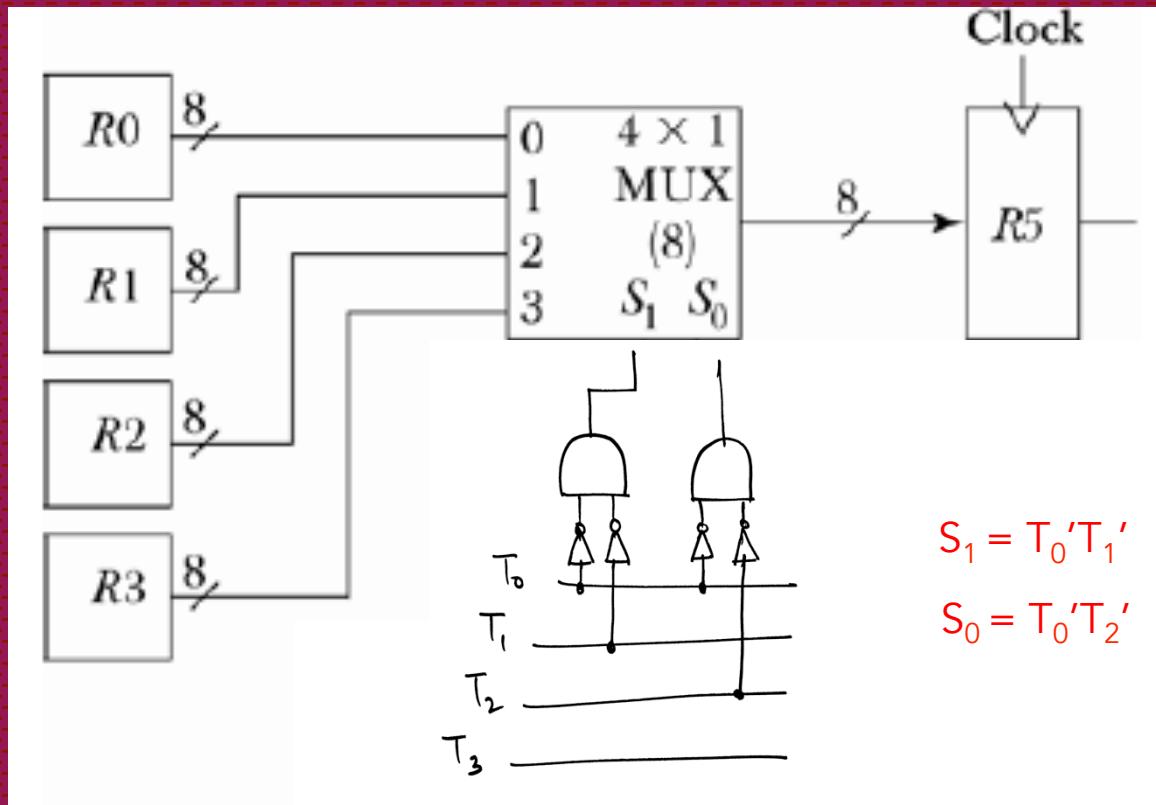Alternative Solution (Using SOP Simplification)



Solution: Step 7

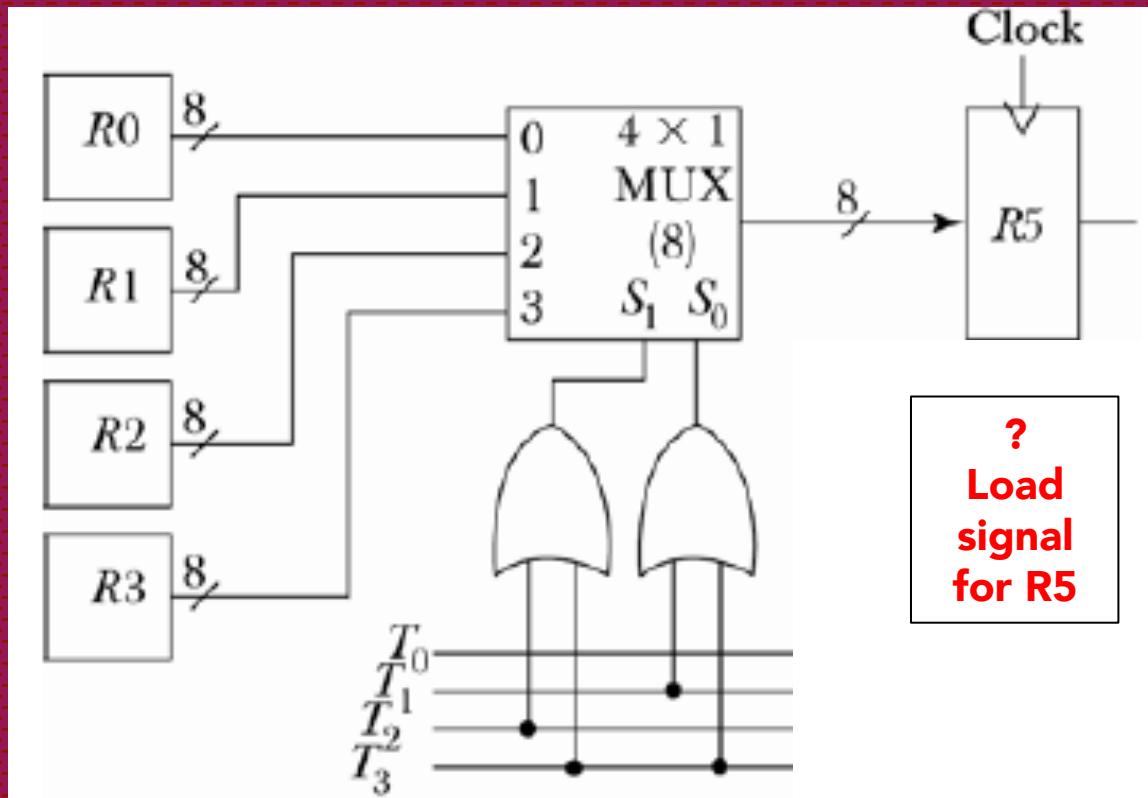

Solution: Step 7

What about the load signal for R5?


$$\text{Load} = T_0 + T_1 + T_2 + T_3$$

R5 must be connected to all the timing signals (since different timing signals enable different registers to transfer their contents to R5).

Also, only one of the timing signals will be 1 at any given time, and we want the load signal of R5 to be 1 for every timing signal.

So, we have to use an OR gate.

Solution: Step 7

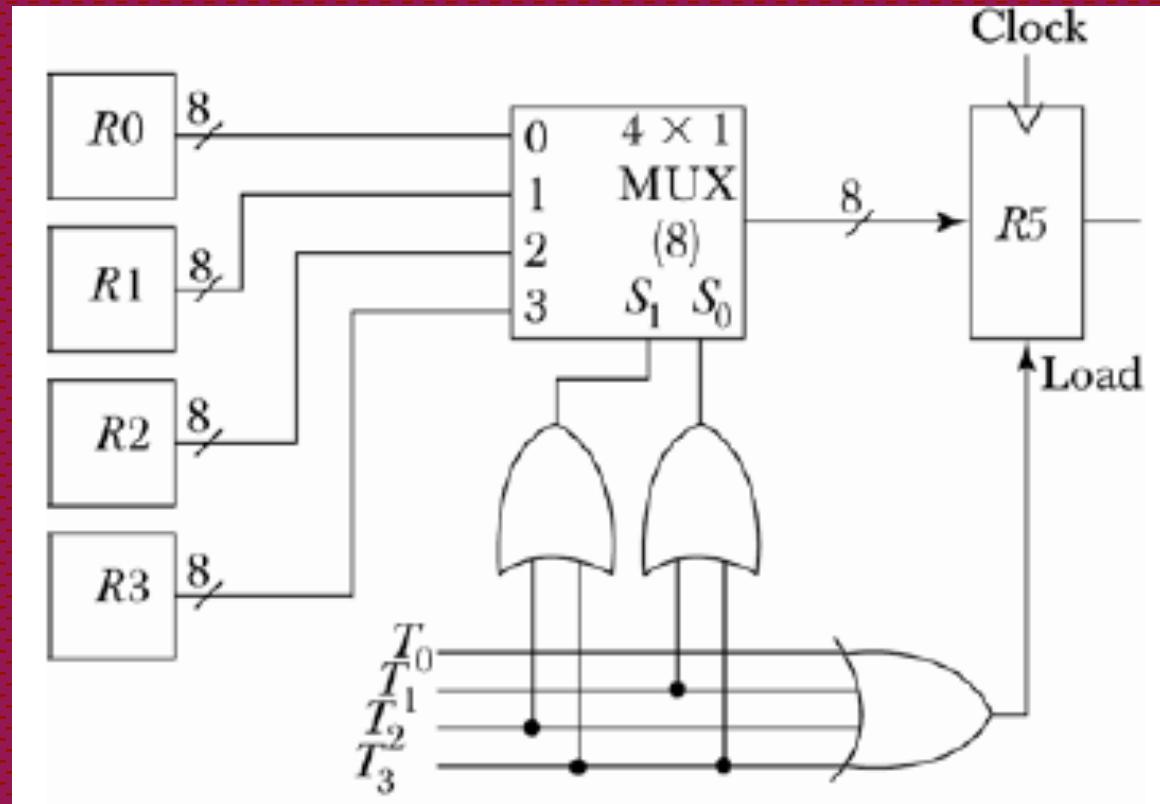

3. Represent the following conditional control statement by two register transfer statements with control functions.


If ($P=1$) then ($R1 \leftarrow R2$) else if ($Q=1$) then ($R1 \leftarrow R3$)

Solution:

$P: R1 \leftarrow R2$

$P'Q: R1 \leftarrow R3$

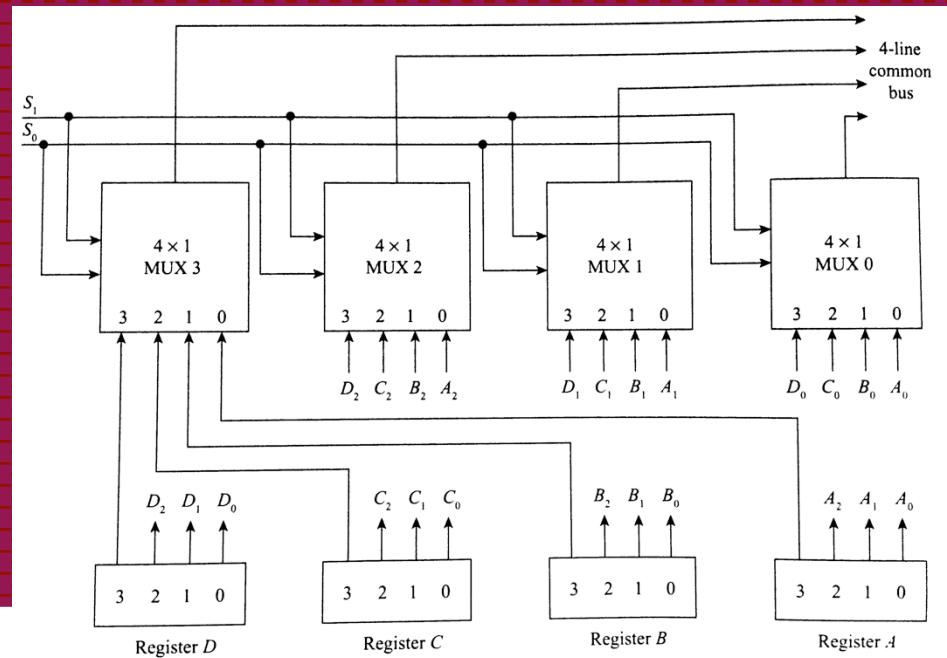4. What has to be done to the bus system in the following figure to be able to transfer information from any register to any other register? Specifically, show the connections that must be included to provide a path from the outputs of register C to the inputs of register A.




Solution:

Connect the 4-line common bus to the four inputs of each register.


Provide “load control” and
“clock” inputs for each register.

To transfer from C to A:

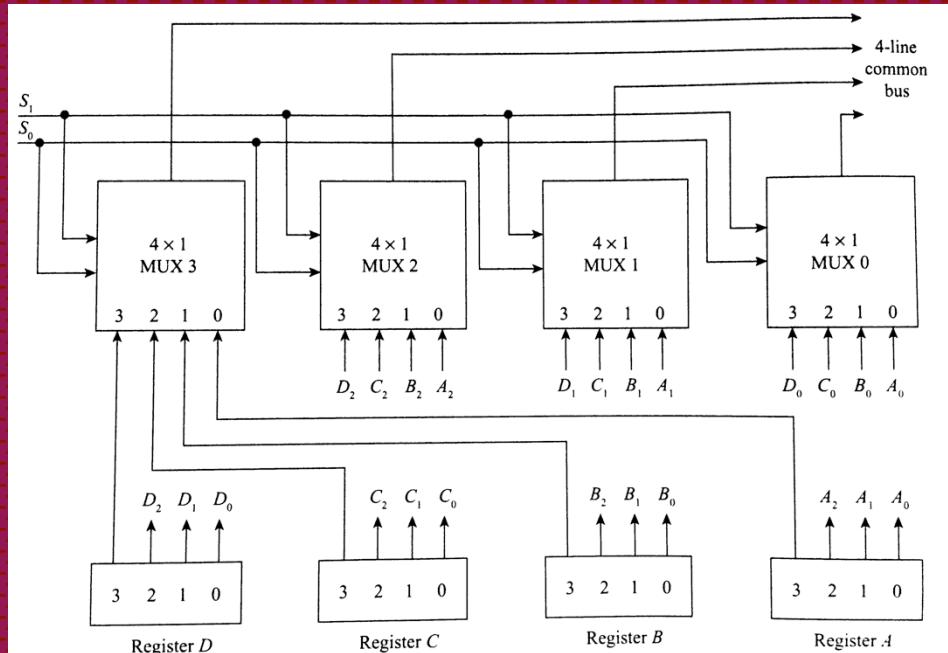
1. Apply $S_1S_0 = 10$
(to select C for the bus.)
2. Enable the load input of A
3. Apply a clock pulse.




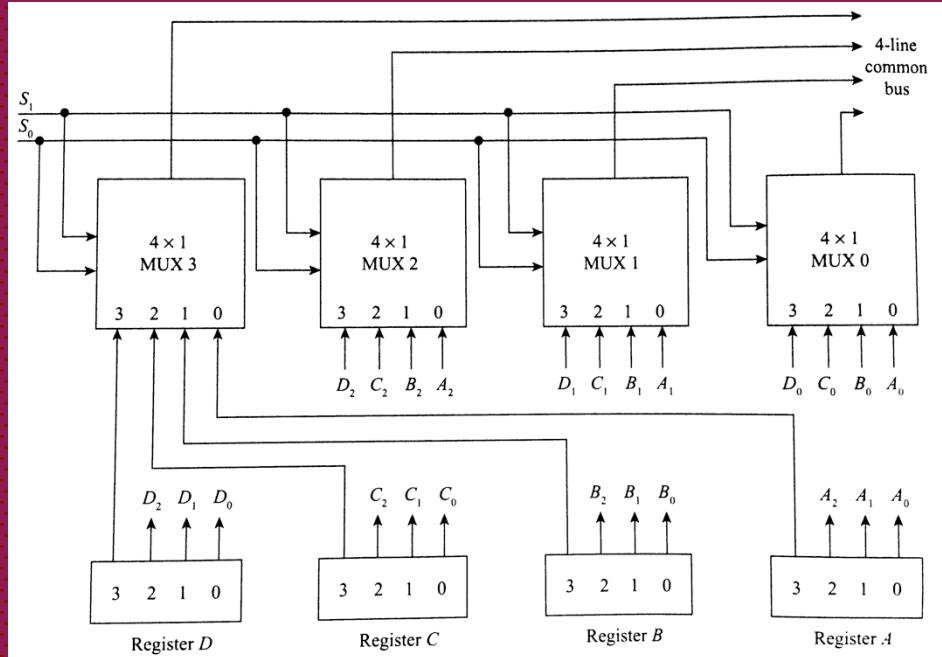
5. Draw a diagram for a bus system similar to the one shown in the following figure, but use three-state buffers and a decoder instead of the multiplexers.



Solution:

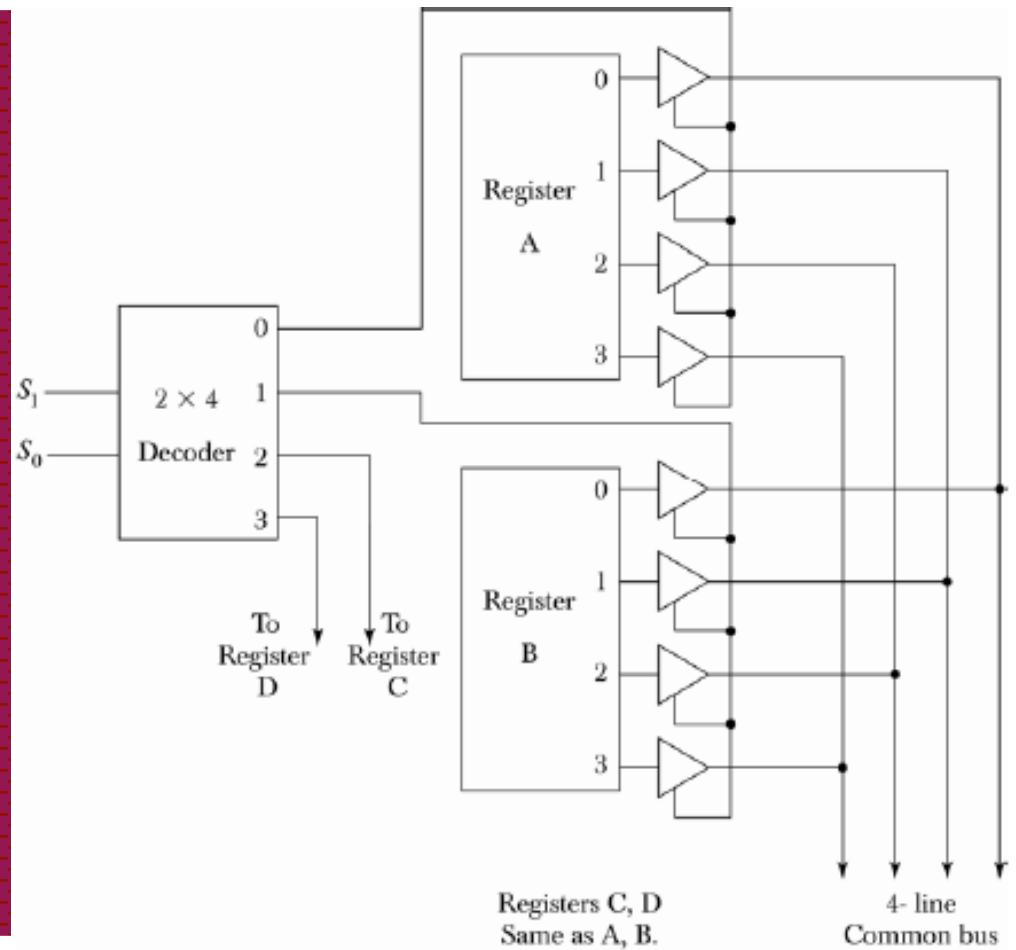

Solution:

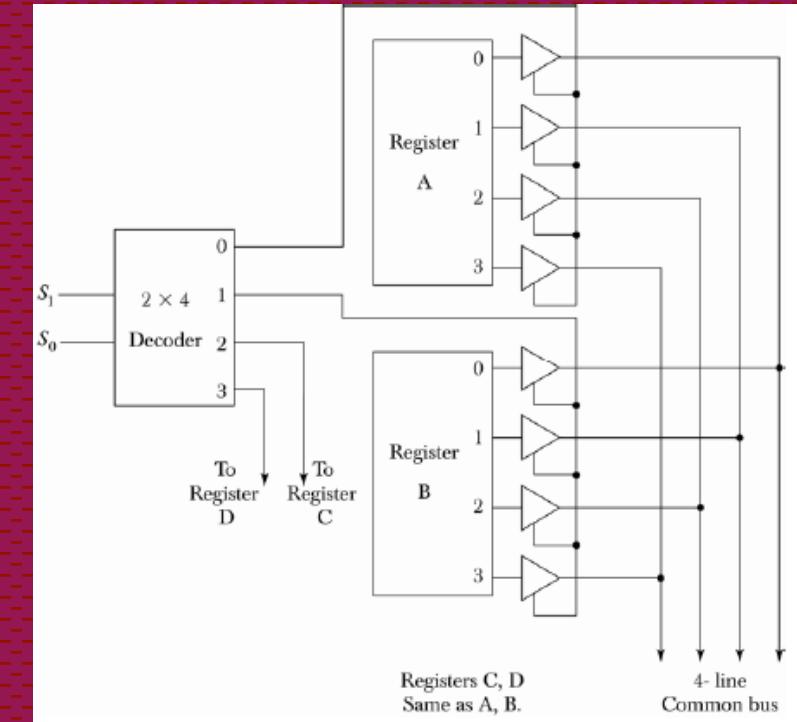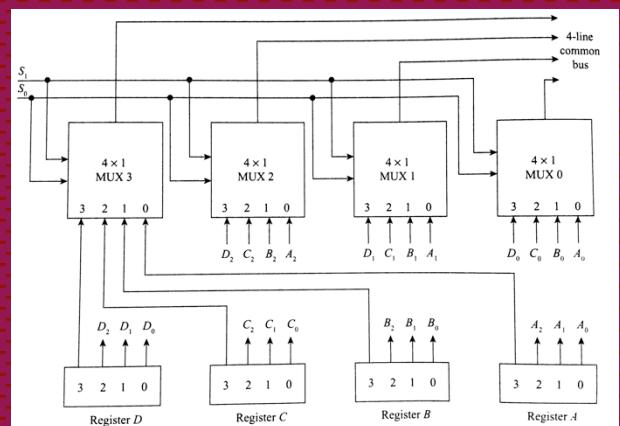

6. A digital computer has a common bus system for 16 registers of 32 bits each. The bus is constructed using multiplexers.
- a. What size of multiplexers are needed?
 - b. How many selection inputs are there in each multiplexer?
 - c. How many multiplexers are there in the bus system?

Solution:

a. What size of multiplexers are needed?

16×1

b. How many selection inputs are there in each multiplexer?

4 selection lines (because $2^4=16$)

c. How many multiplexers are there in the bus system?

32 (one for each bit of the registers).

7. The following transfer statement specify a memory. Explain the memory operation in each case.

a. $R2 \leftarrow M[AR]$

b. $M[AR] \leftarrow R3$

c. $R5 \leftarrow M[R5]$

Solution:

a. $R2 \leftarrow M[AR]$

Read the memory word specified by the address in AR into R2.

b. $M[AR] \leftarrow R3$

Write the contents of R3 into the memory word specified by the address in AR.

c. $R5 \leftarrow M[R5]$

Read the memory word specified by the address in R5 into R5. (This will overwrite the previous value of R5.)

8. Draw a block diagram of the hardware that implements the following register transfer statement:


$$x+yz: AR \leftarrow AR+BR$$

AR and *BR* are two *n*-bit registers, and *x*, *y*, *z* are control variables. Include the logic gates for the control functions.

Remember that a + sign denotes an OR operation in a control or Boolean function but it represents an arithmetic plus in a microoperation.


Solution: Step 1

$$x+yz: AR \leftarrow AR+BR$$

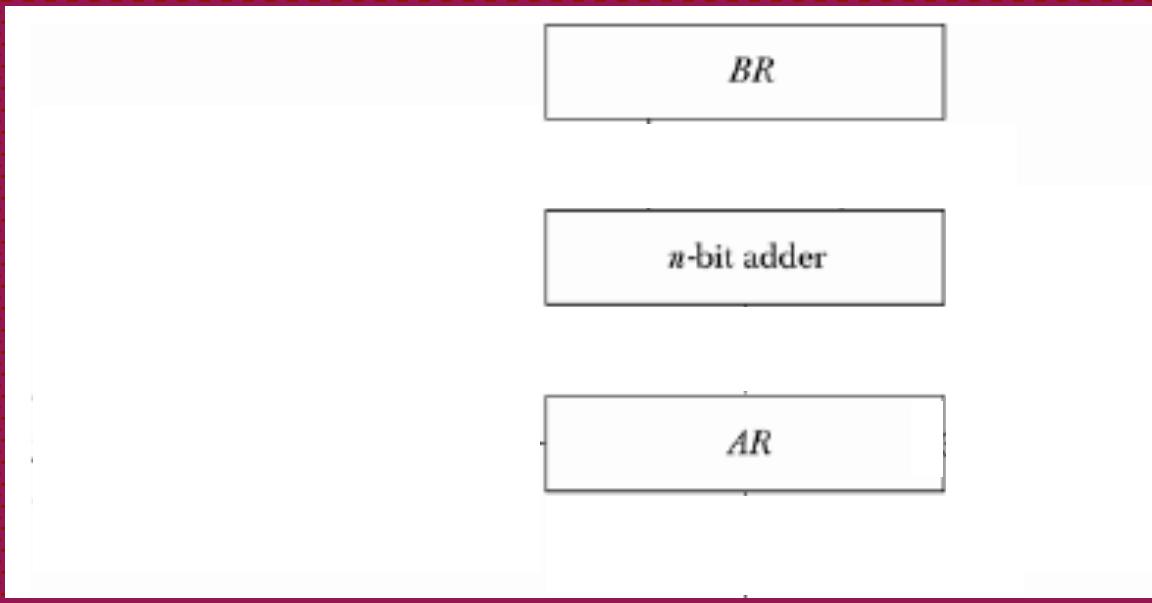


Solution: Step 2

$$x+yz: AR \leftarrow AR+BR$$

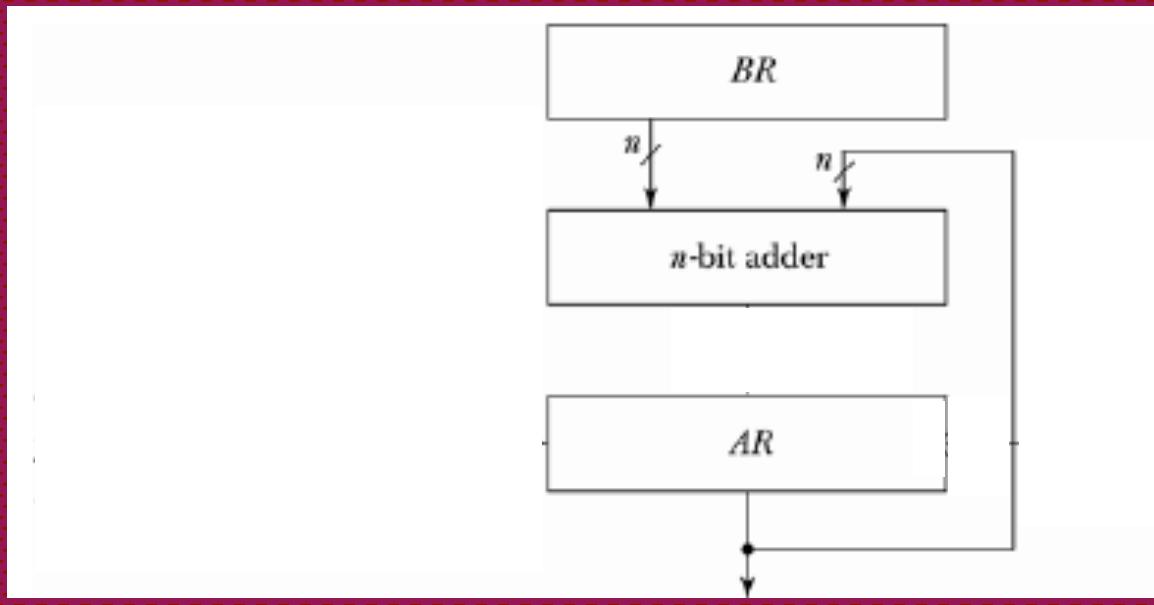


Solution: Step 3

$$x+yz: AR \leftarrow AR+BR$$

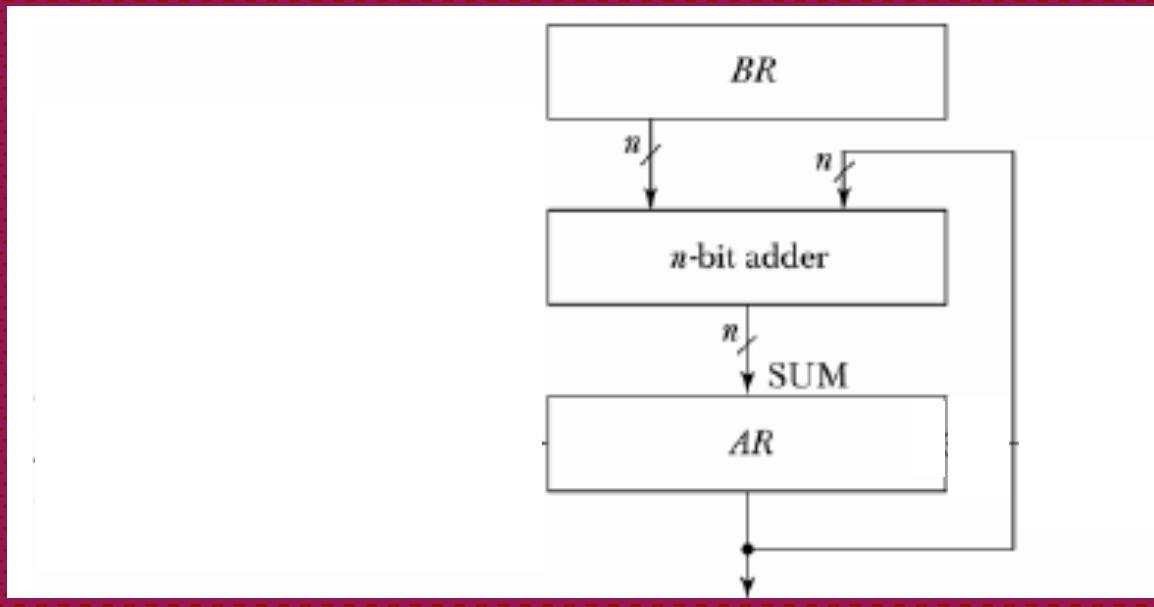


Solution: Step 4

$$x+yz: AR \leftarrow AR+BR$$

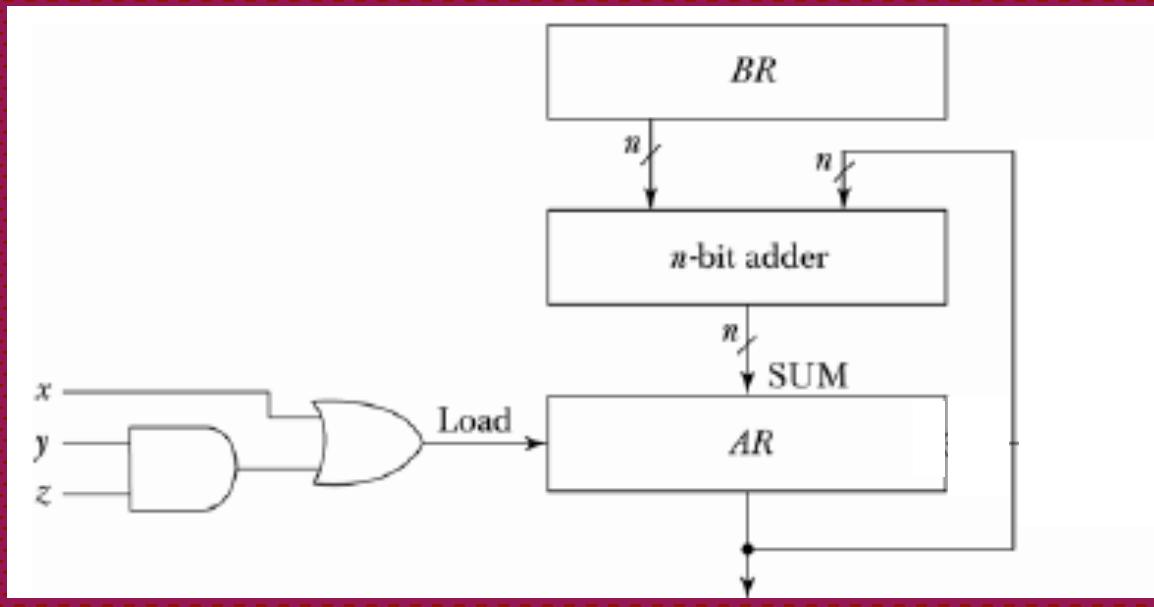

Solution: Step 5

$$x+yz: AR \leftarrow AR+BR$$

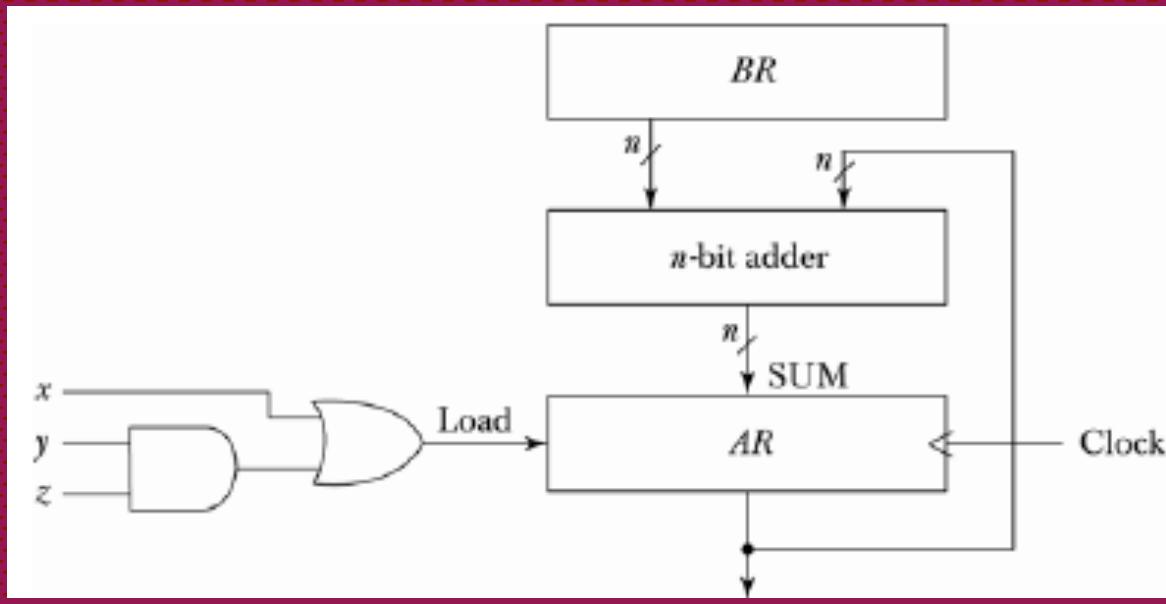


9. Show the hardware that implements the following statement:

$$xyT_0 + T_1 + y'T_2 : AR \leftarrow AR + 1$$

Include the logic gates for the control function and a block diagram for a binary counter with a count enable input.



Solution: Step 1

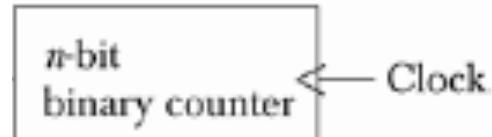$xyT_0 + T_1 + y'T_2: [AR \leftarrow AR+1] \rightarrow \text{Binary Counter}$





Solution: Step 2
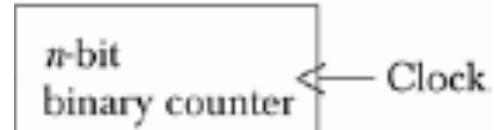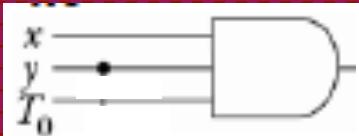
$$xyT_0 + T_1 + y'T_2: AR \leftarrow AR+1$$




Solution: Step 3
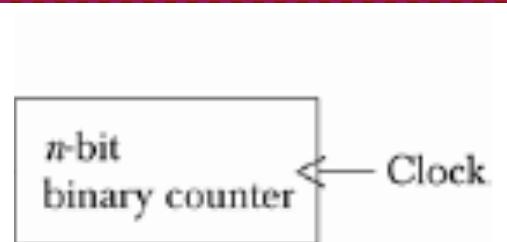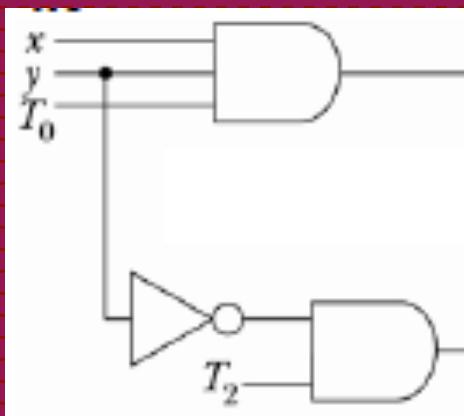
$$xyT_0 + T_1 + y'T_2: AR \leftarrow AR+1$$



Solution: Step 4
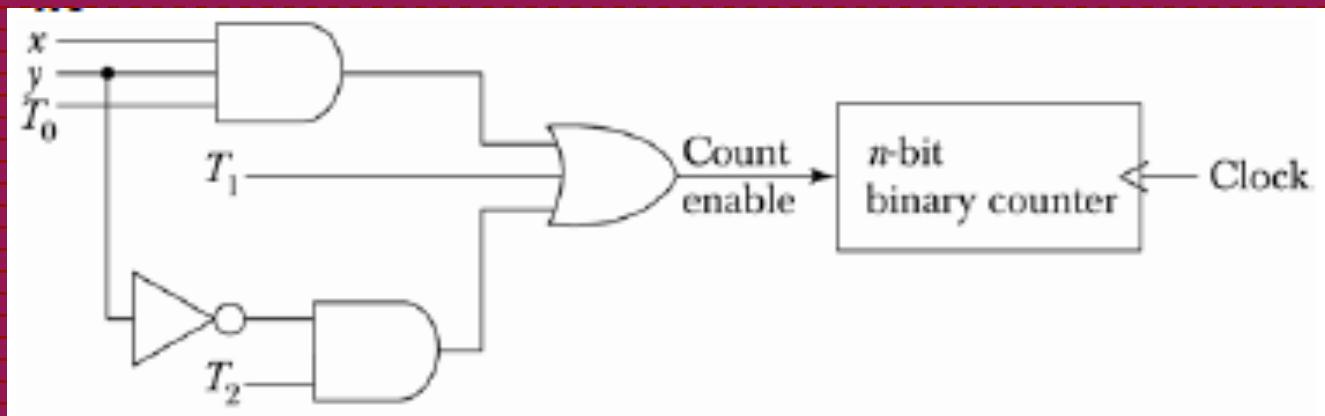
$$xyT_0 + T_1 + y'T_2: AR \leftarrow AR+1$$



10 . Consider the following register transfer statements for two 4-bit registers $R1$ and $R2$:

$$xT: R1 \leftarrow R1 + R2$$

$$x'T: R1 \leftarrow R2$$

Every time $T=1$, either the contents of $R2$ are added to the contents of $R1$ (if $x=1$), or the contents of $R2$ are transferred to $R1$ (if $x=0$). Draw a diagram showing the hardware implementation of the two statements. Use block diagrams for the registers, a 4-bit adder, and a quadruple 2-to-1 line mux that selects the inputs to $R1$. In the diagram, show how x and T select the inputs of the mux and the load input of $R1$.

Solution: Step 1

$xT: R1 \leftarrow R1 + R2$



$x'T: R1 \leftarrow R2$



Solution: Step 2

$$xT: R1 \leftarrow R1 + R2$$


$$x'T: R1 \leftarrow R2$$

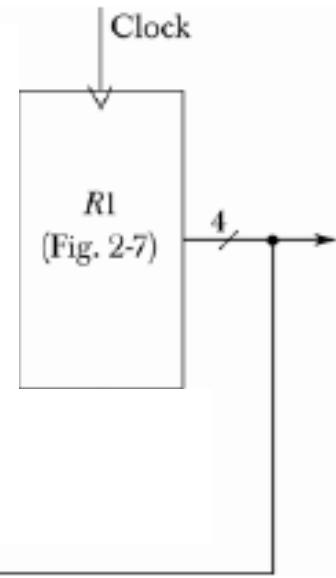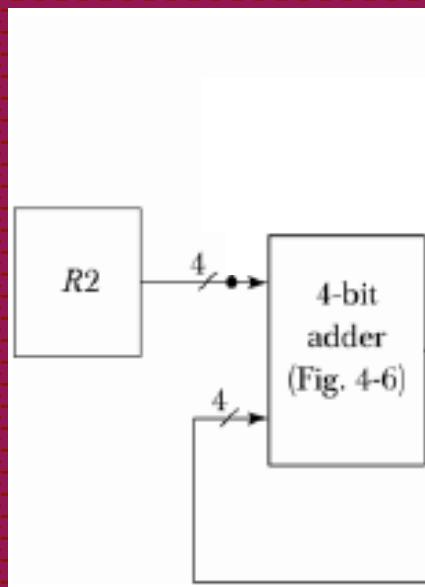

Solution: Step 3

$$xT: R1 \leftarrow R1 + R2$$


$$x'T: R1 \leftarrow R2$$

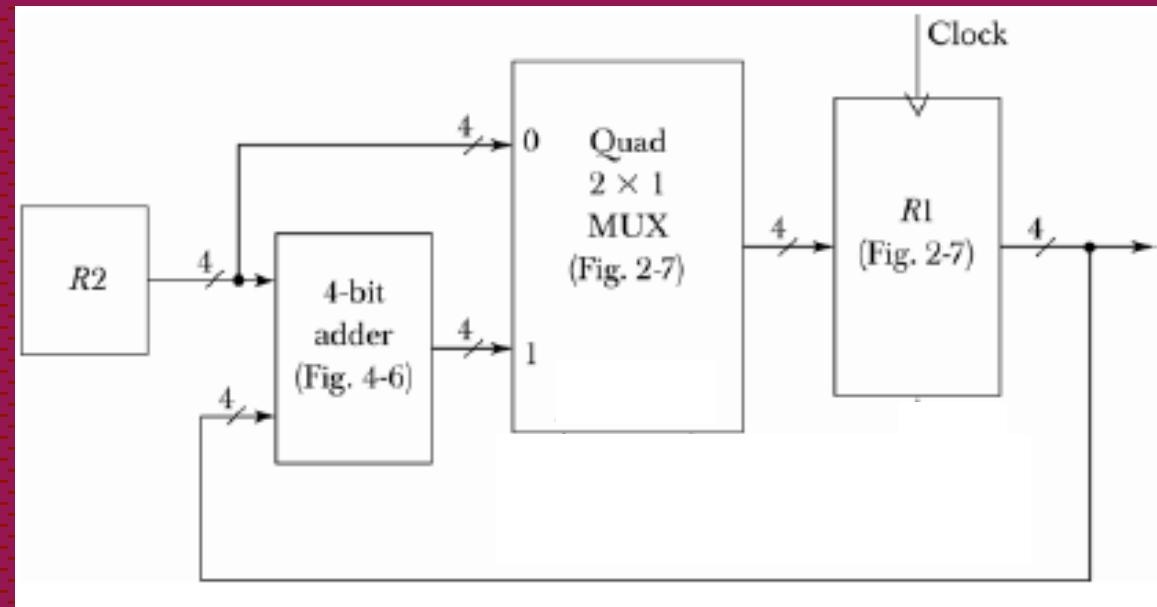

Solution: Step 4

$$xT: R1 \leftarrow R1 + R2$$


$$x'T: R1 \leftarrow R2$$

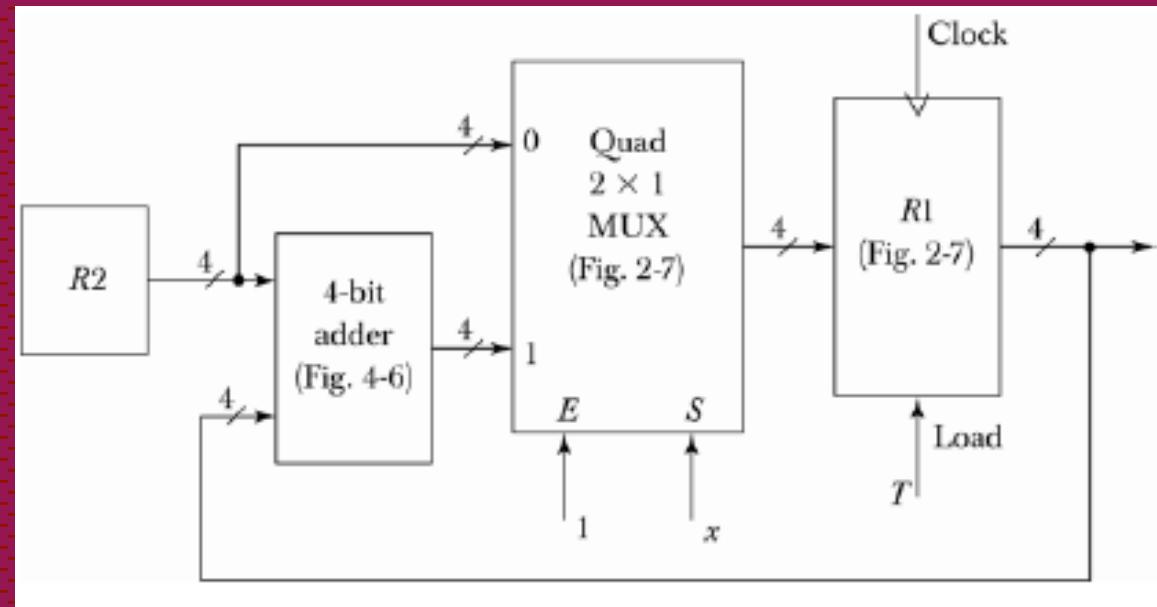

12. The adder-subtractor circuit shown below has the following values for input mode M and data inputs A and B . In each case, determine the values of the outputs S_3 , S_2 , S_1 , S_0 , and C_4 .

M	A	B
0	0111	0110
0	1000	1001
1	1100	1000
1	0101	1010
1	0000	0001

Adder-Subtractor

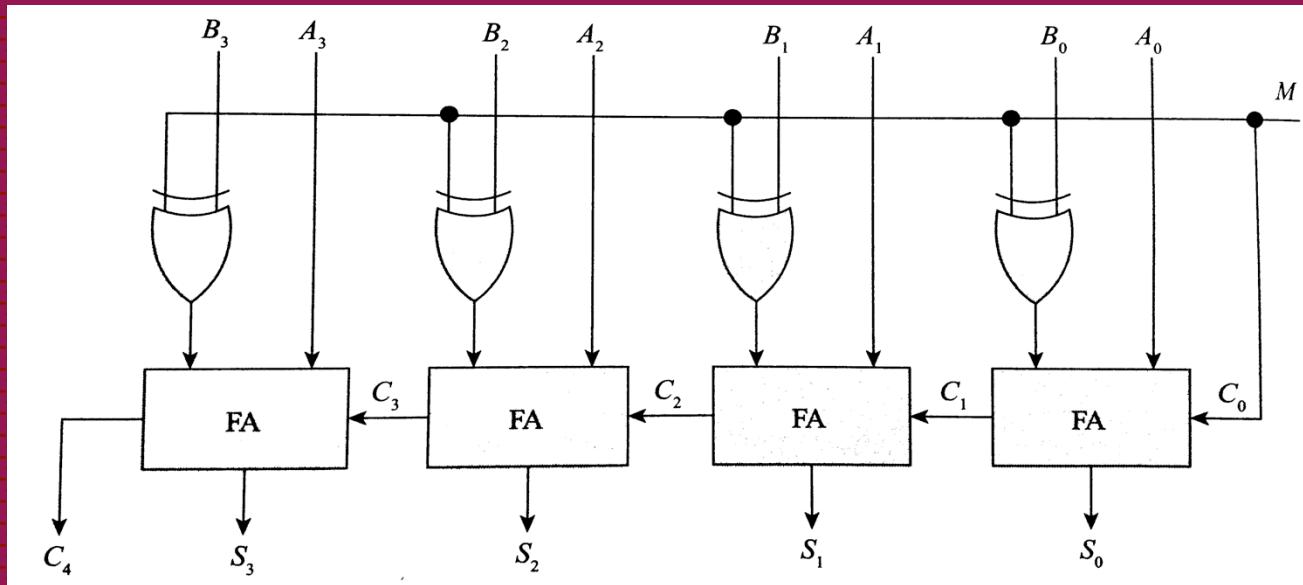

Solution:

When mode $M = 0$, the circuit acts as an adder.

When $M= 1$, the circuit acts as a subtractor. (subtraction in 2's complement form)


M	A	B	Sum/Difference	Carry (C_4)
0	0111	0110	$0111 + 0110 = 1101$	0
0	1000	1001	$1000 + 1001 = 0001$	1
1	1100	1000	$1100 - 1000 = 0100$	1
1	0101	1010	$0101 - 1010 = 1011$	0
1	0000	0001	$0000 - 0001 = 1111$	0

13. Design a 4-bit combinational circuit decrementer using four full-adders.

Solution: A decrementer operates by subtracting 1 from the given number, i.e., it adds (-1) to the number.

$$\text{So, } A - 1 = A + (\text{2's complement of 1}) = A + 1111 \longrightarrow$$

A_3	A_2	A_1	A_0
+ 1	1	1	1

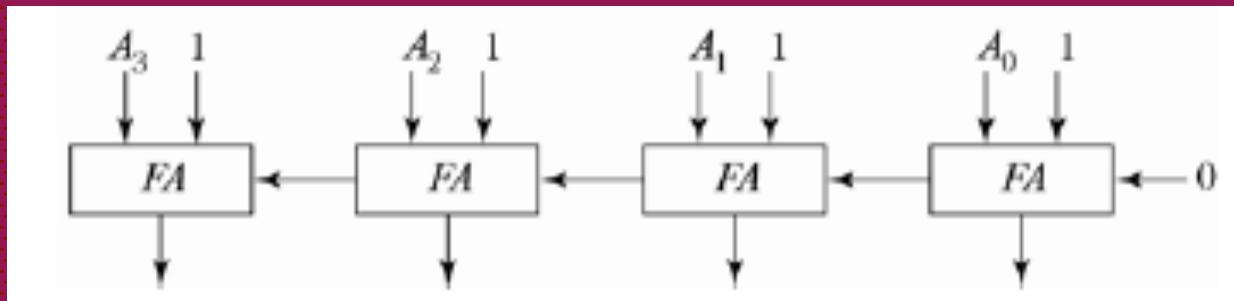

14. Assume that the following


4-bit arithmetic circuit is enclosed

in a single IC package.


Show the connections among two

such ICs that form an 8-bit


arithmetic circuit.

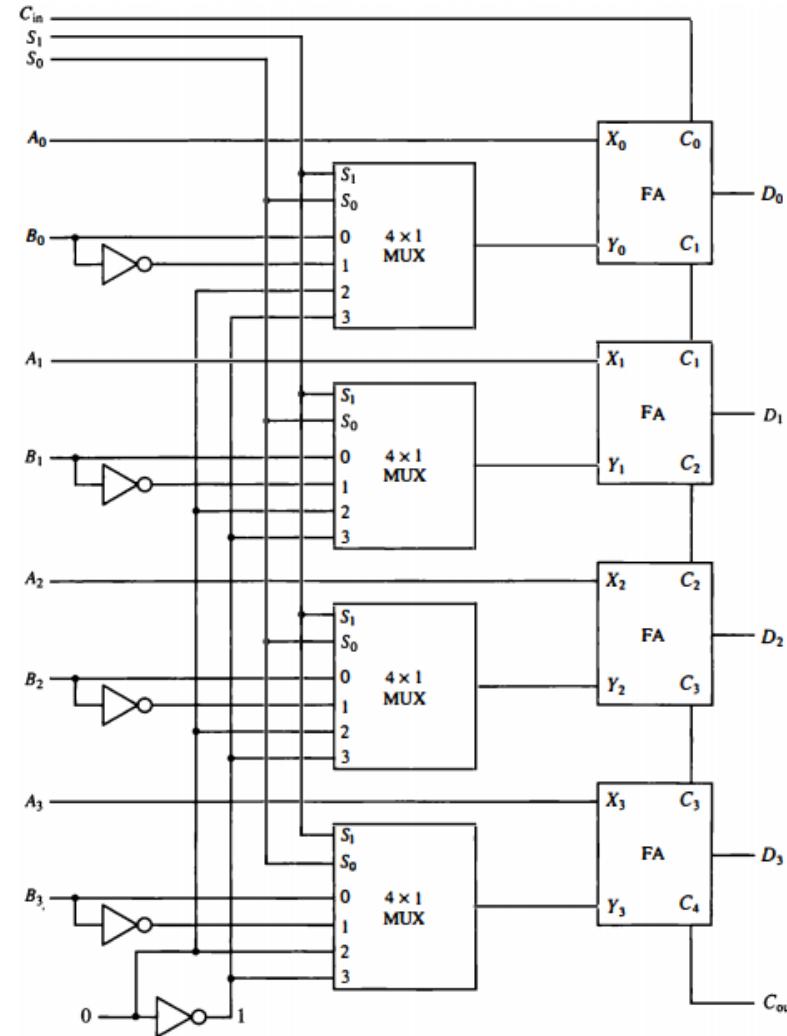

Solution:

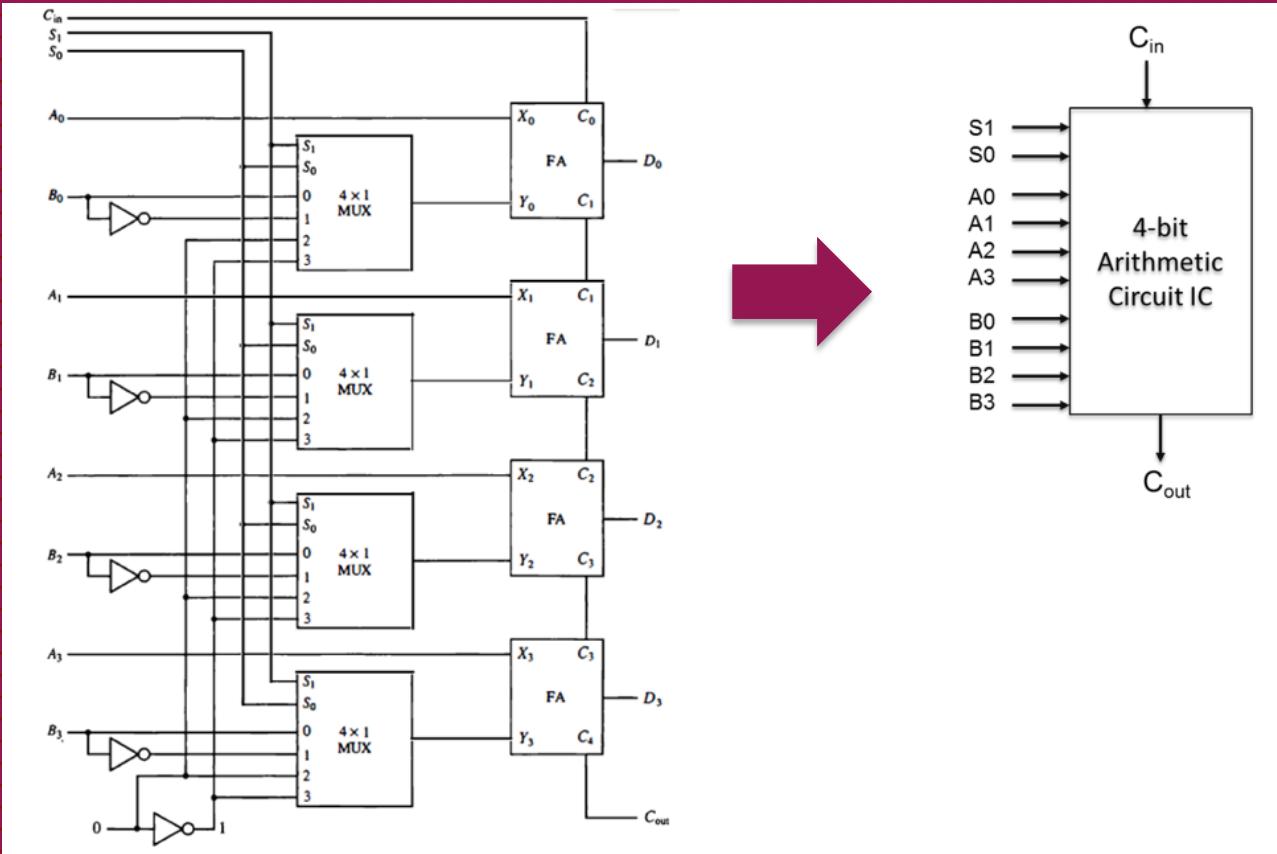

Solution:

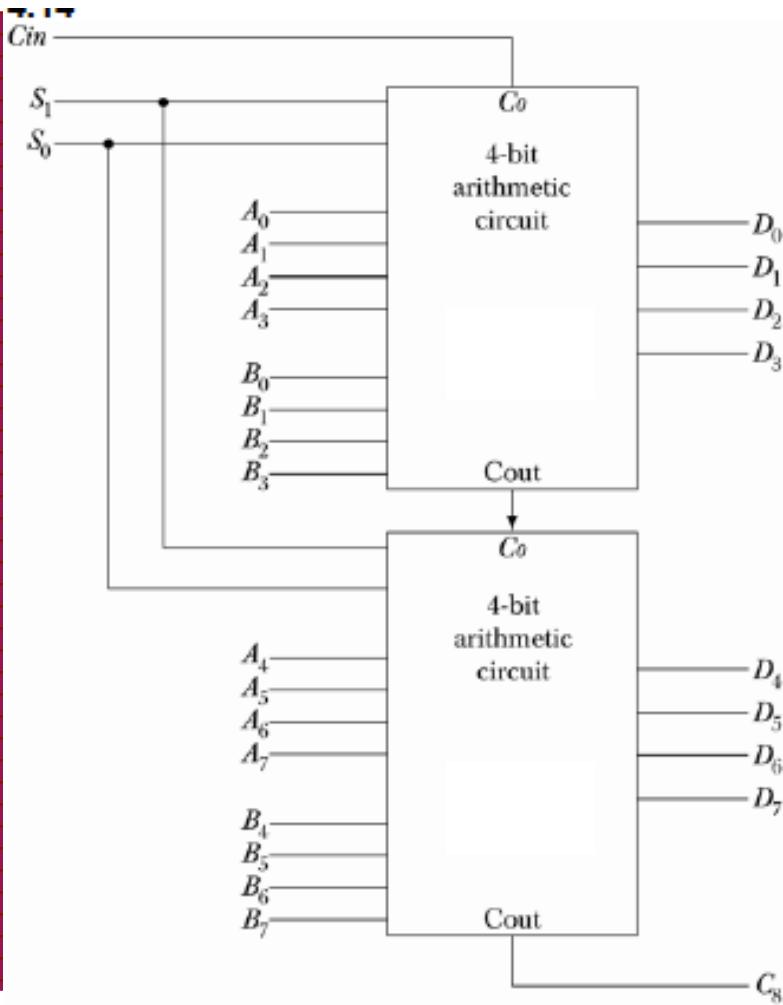

15. Design an arithmetic circuit with one selection variable S and two n -bit data inputs A and B . the circuit generates the following four arithmetic operations in conjunction with the input carry C_{in} . Draw a logic diagram for the first two stages.

S	$C_{in} = 0$	$C_{in} = 1$
0	$D = A + B$	$D = A + 1$
1	$D = A - 1$	$D = A + B' + 1$

Solution: Let's gather some clues about the kind of circuit we need to draw.

S	$C_{in} = 0$	$C_{in} = 1$
0	$D = A + B$	$D = A + 1$
1	$D = A - 1$	$D = A + B' + 1$

Essentially, we need to perform addition, so we have to use an **adder**.

There is also a carry, so we have to use a **full-adder**.

In each of the four operations, one of the operands is always A , and the second operand keeps changing. So, one of the inputs to the FA should be A and the second input should come from a **multiplexer** (this will also take care of the selection variable).

Solution: Step 1

Let's convert the given table into a truth table for the new circuit.


S	$C_{in} = 0$	$C_{in} = 1$
0	$D = A + B$	$D = A + 1$
1	$D = A - 1$	$D = A + B' + 1$



S	C_{in}	X	Y
0	0	A	B
0	1	A	0
1	0	A	1
1	1	A	B'


Solution: Step 2

S	C _{in}	X	Y
0	0	A	B
0	1	A	0
1	0	A	1
1	1	A	B'

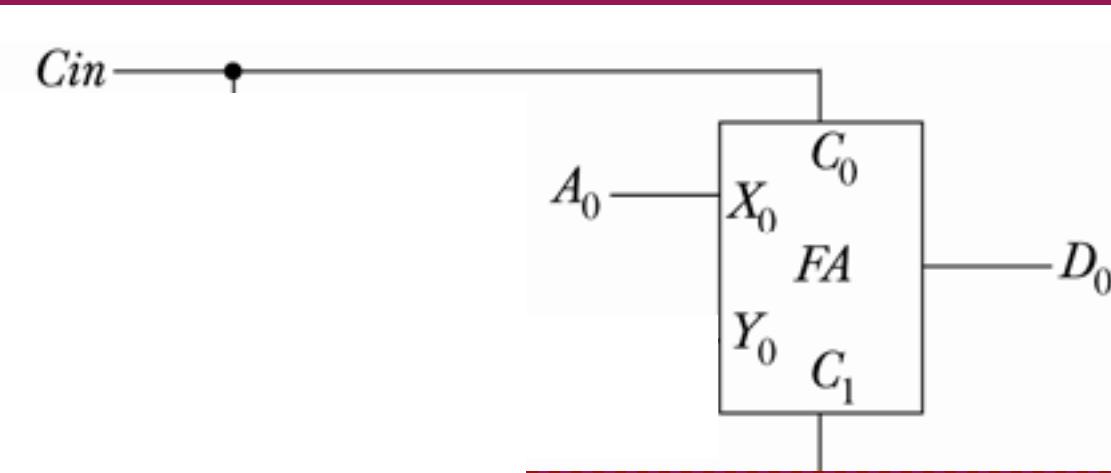


Solution: Step 3

S	C_{in}	X	Y
0	0	A	B
0	1	A	0
1	0	A	1
1	1	A	B'

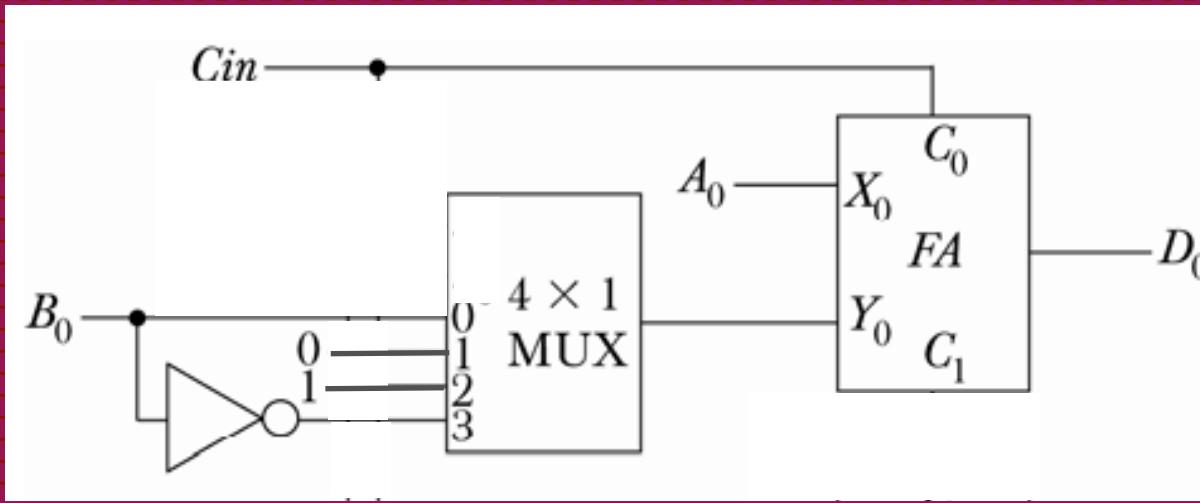


Solution: Step 4

S	C_{in}	X	Y
0	0	A	B
0	1	A	0
1	0	A	1
1	1	A	B'

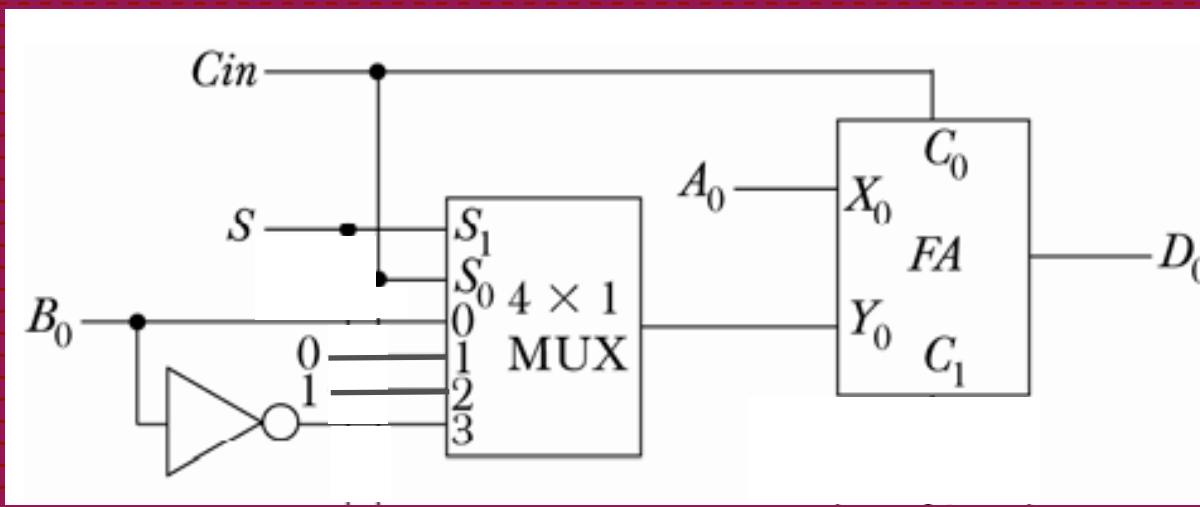


Solution: Step 5

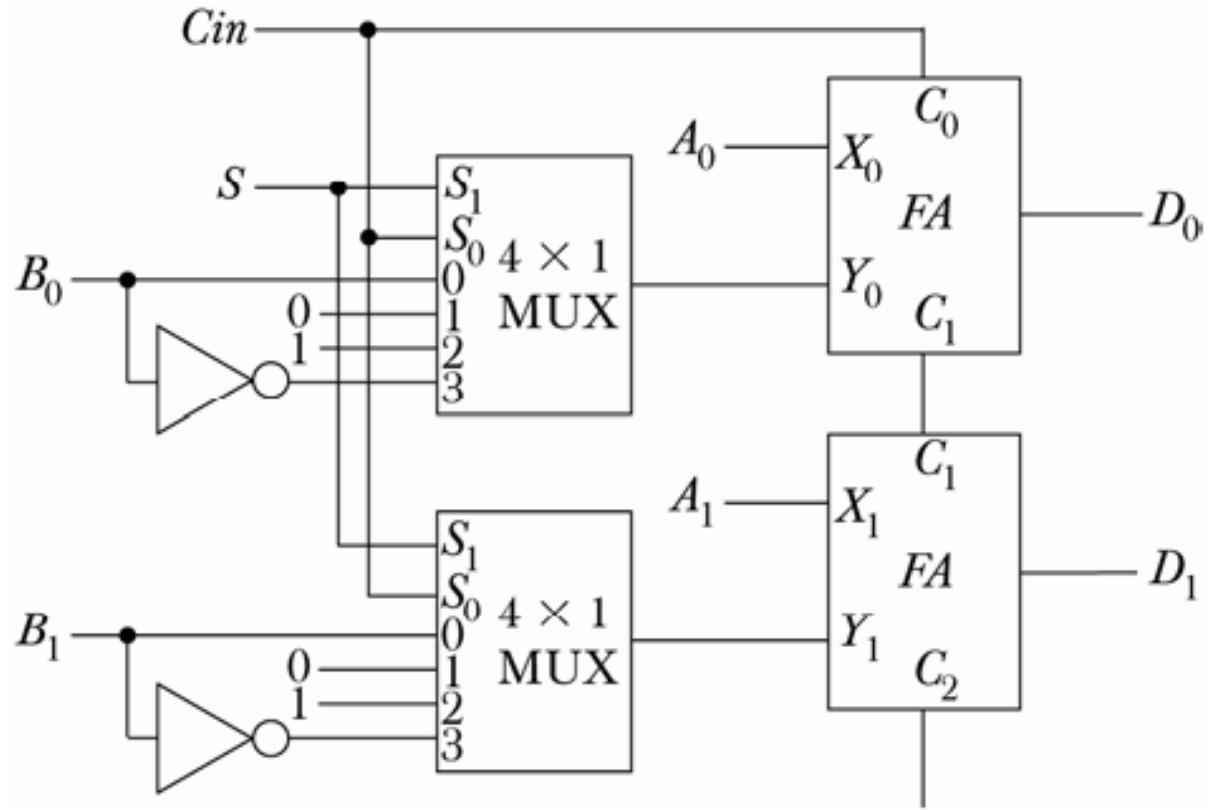

16. Design a combinational circuit that selects and generates any of the 16 logic functions listed in the following table.

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1	
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	1	

Solution:

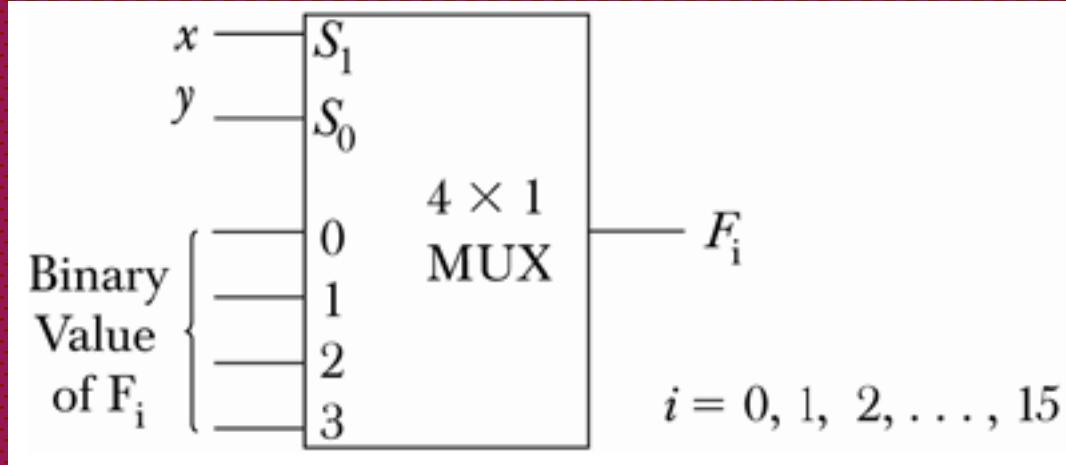

17. Design a digital circuit that performs the four logic operations (Exclusive-OR, Exclusive-NOR, NOR, and NAND). Use two selection variables and show the logic diagram for a typical stage.


Solution: Step 1

Let's first generate a function table for the circuit.


S_1	S_0	Function to be performed
0	0	XOR
0	1	XNOR
1	0	NOR
1	1	NAND

Solution: Step 2

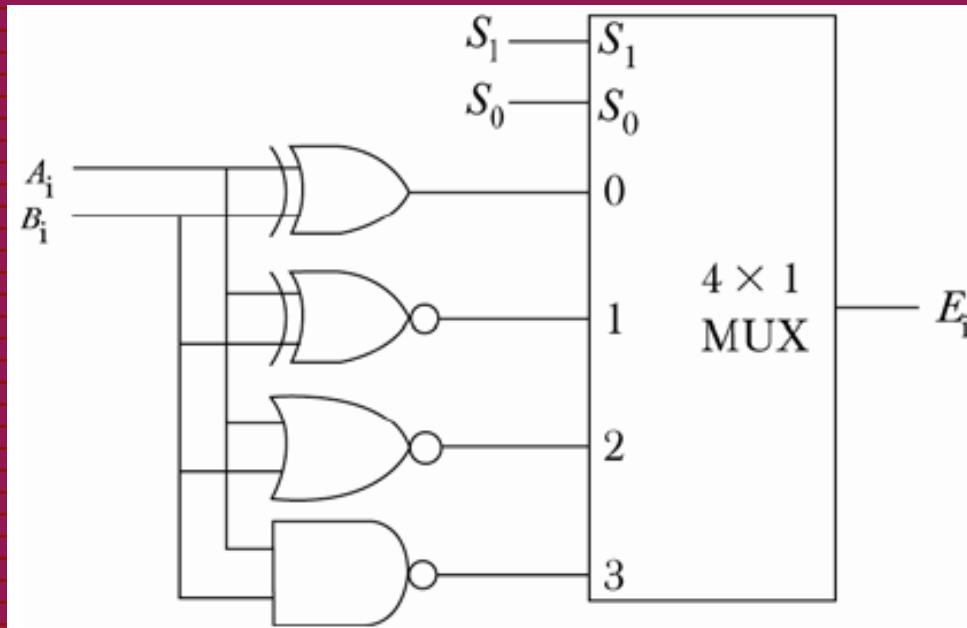Since we need to be able to generate four functions using two selection variables, we will have to use a 4x1 mux.



Solution

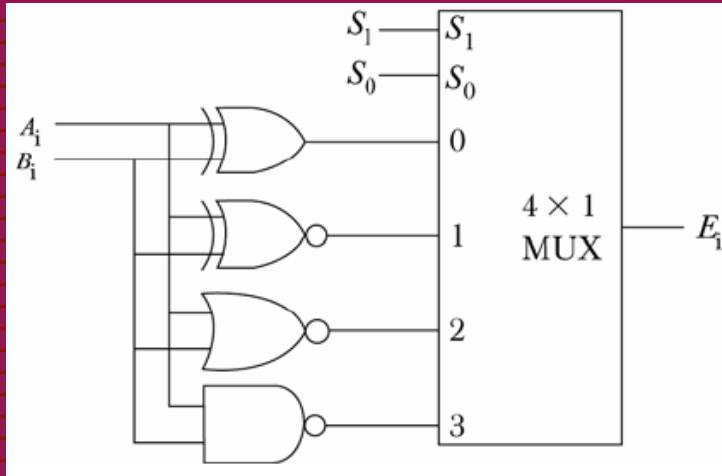

S_1	S_0	E_i
0	0	$A_i \oplus B_i$
0	1	$A_i \oplus \bar{B}_i$
1	0	$\bar{A}_i \oplus B_i$
1	1	$\bar{A}_i \oplus \bar{B}_i$

18. Register A holds the 8-bit binary 11011001. Determine the logic microoperation and the value in the second register B that will cause the value in A to be changed to:

- a. 01101101
- b. 11111101

Solution:

a. XOR operation with $B = 10110100$, followed by register transfer.

$$\begin{array}{r} 11011001 \\ \oplus 10110100 \\ \hline 01101101 \end{array}$$

Value in A Value in B
Result in A after $A \leftarrow A \oplus B$

b. OR operation with $B = 11111101$, followed by register transfer.

$$\begin{array}{r} 11011001 \\ \vee 11111101 \\ \hline 11111101 \end{array}$$

Value in A Value in B
Result in A after $A \leftarrow A \vee B$

19. The 8-bit registers AR, BR, CR, and DR initially have the following values:

$$AR=11110010$$

$$BR=11111111$$

$$CR=10111001$$

$$DR=11101010$$

Determine the 8-bit values in each register after the execution of the following sequence of microoperations.

a. $AR \leftarrow AR + BR$ (**Add BR to AR**)

b. $CR \leftarrow CR \wedge DR$, $BR \leftarrow BR + 1$ (**AND DR and CR, increment BR**)

c. $AR \leftarrow AR - CR$ (**Subtract CR from AR**)

Solution:

a. $\text{AR} \leftarrow \text{AR} + \text{BR}$ (*Add BR to AR*)

$$\begin{array}{r} \text{AR} = 1\ 1\ 1\ 1\ 0\ 0\ 1\ 0 \\ \text{BR} = 1\ 1\ 1\ 1\ 1\ 1\ 1\ 1 \\ \hline \text{AR+BR} = 1\ 1\ 1\ 1\ 0\ 0\ 0\ 1 \end{array}$$

So, $\text{AR} = 11110001$, $\text{BR} = 11111111$, $\text{CR} = 10111001$, $\text{DR} = 11101010$

Solution:

b. $CR \leftarrow CR \wedge DR$, $BR \leftarrow BR + 1$ (AND DR and CR, increment BR)

$$CR = 10111001$$

$$DR = 11101010$$

$$CR \wedge DR = 10101000$$

$$BR = 11111111$$

$$+ 1$$

$$BR + 1 = 00000000$$

So, AR = 11110001, BR = 00000000, CR = 10101000, DR = 11101010

Solution:

c. $AR \leftarrow AR - CR$ (*Subtract CR from AR*)

$$AR = 1\ 1\ 1\ 1\ 0\ 0\ 0\ 1$$

$$CR = 1\ 0\ 1\ 0\ 1\ 0\ 0\ 0$$

$$AR - CR = 0\ 1\ 0\ 0\ 1\ 0\ 0\ 1$$

So, $AR = 01001001$, $BR = 00000000$, $CR = 10101000$, $DR = 11101010$

20. An 8-bit register contains the binary value 10011100. What is the register value after an arithmetic shift-right?

Starting from the initial number 10011100, determine the register value after an arithmetic shift-left, and state whether there is an overflow.

Solution:

$$R = 10011100$$

After Arithmetic Shift-Right 11001110

After Arithmetic Shift-Left 00111000 : overflow occurs because the number, which was originally negative, becomes positive after the shift.

21. Starting from the initial value of $R = 11011101$, determine the sequence of binary values in R after a logical shift-left, followed by a circular shift-right, followed by a logical shift-right, and a circular shift-left.

Solution:

$$R = 11011101$$


After Logical Shift-Left 10111010

After Circular Shift-Right 01011101

After Logical Shift-Right 00101110

After Circular Shift-Left 01011100

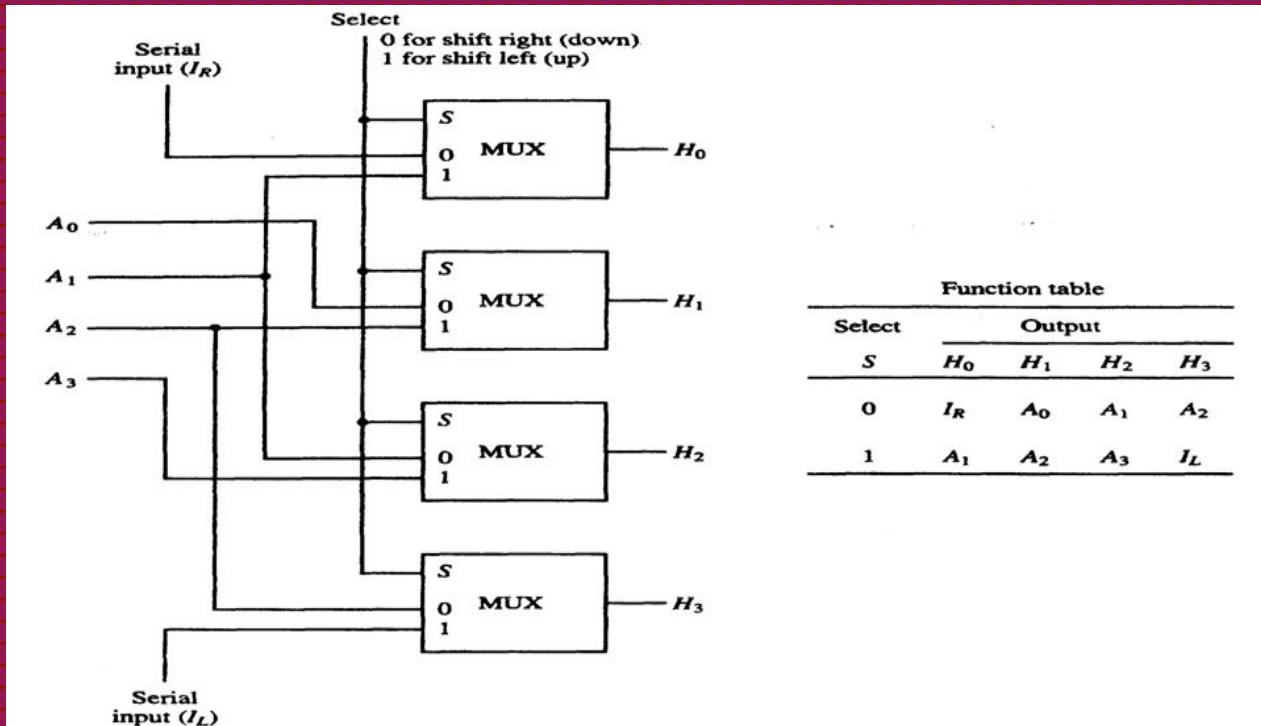22. What is the value of output H in the following figure if input A is 1001, $S = 1$, $I_r = 1$, and $I_L = 0$?



Solution: The given circuit is a 4-bit combinational circuit shifter.

$S = 1$ will cause it to perform a **left-shift**.

The given input is $A = 1\ 0\ 0\ 1$, i.e., $A_0 = 1$, $A_1 = 0$, $A_2 = 0$, and $A_3 = 1$.

Since the circuit will perform a left-shift, its output (according to the below mentioned function table) should be:

Function table					
Select	Output				
	H_0	H_1	H_2	H_3	
0	I_R	A_0	A_1	A_2	
1	A_1	A_2	A_3	I_L	

$A_1\ A_2\ A_3\ I_L$

i.e.,

0 0 1 0

23. What is wrong with the following register transfer statements?

- a. $xT: AR \leftarrow \overline{AR}, AR \leftarrow 0$
- b. $yT: R1 \leftarrow R2, R1 \leftarrow R3$
- c. $zT: PC \leftarrow AR, PC \leftarrow PC + 1$

Solution

a. $xT: AR \leftarrow AR, AR \leftarrow 0$

The two microoperations -Compliment and Clear - are supposed to be done at the same time on the same register, this is wrong coz these microoperations can't be implemented on the same register at the same time.

b. $yT: R1 \leftarrow R2, R1 \leftarrow R3$

Two different values cannot be transferred to the same register at the same time.

c. $zT: PC \leftarrow AR, PC \leftarrow PC + 1$

It is not possible to move a new value into a register (PC) and increment that value at the same time.